

# Phasor Circuit Analysis

## Phasor Diagrams, Voltage and Current Division

# Phasor Diagram


Phasors are denoted by vectors in 2-D space. Phasor diagrams graphically illustrate the summation of complex values

Consider the following summation of complex numbers resulting from setting up a KVL or KCL equation:

$$7\angle 0 = 9\angle -45^\circ + 6.4\angle 84.29^\circ$$


$$7 = 9\cos(-\pi 45/180) + j9\sin(-\pi 45/180) + 6.4\cos(\pi 84.29/180) + j6.4\sin(\pi 84.29/180)$$

$$7 = 6.36 - j6.36 + 0.64 + j6.36$$

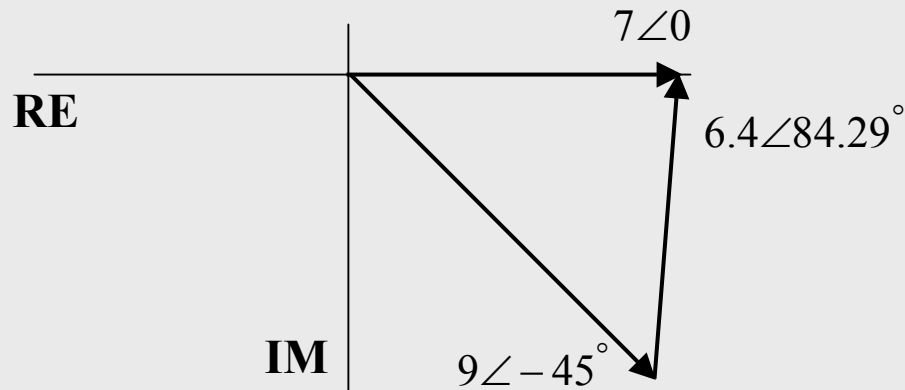

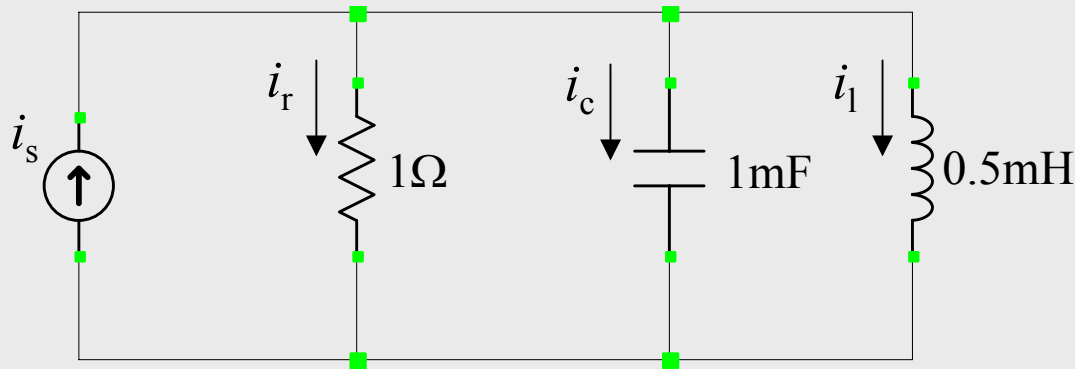
# Phasor Diagram Example

Draw Currents  $i_s$ ,  $i_r$ ,  $i_l$ ,  $i_c$  in a phasor diagram to show  $i_s = i_r + i_l + i_c$  where  $i_s(t) = \sin(1000t)$  A



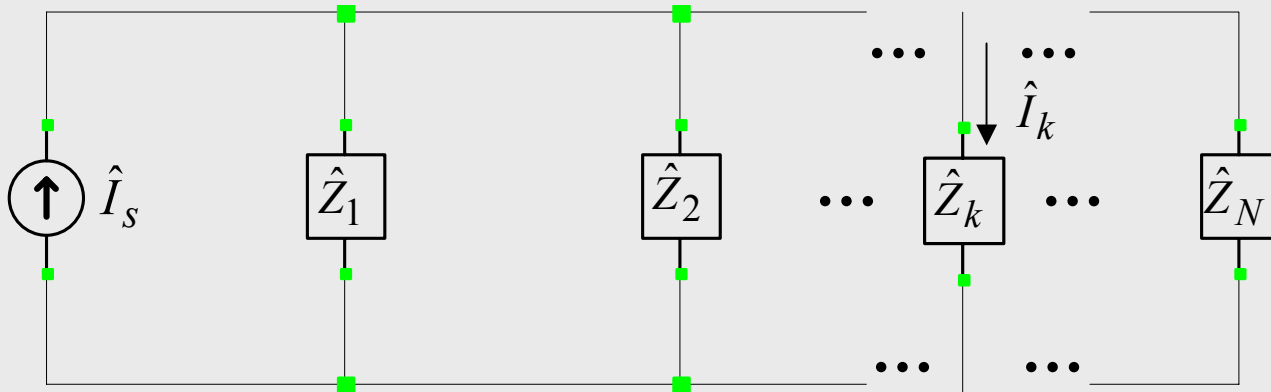
# Current Division

By substituting impedance in for resistance (or admittance for conductance), the current division formula can be generalized to:



$$\hat{I}_k = \hat{I}_s \frac{\frac{1}{\hat{Z}_k}}{\frac{1}{\hat{Z}_1} + \frac{1}{\hat{Z}_2} + \dots + \frac{1}{\hat{Z}_k} + \dots + \frac{1}{\hat{Z}_N}} = \hat{I}_s \frac{\hat{Y}_k}{\hat{Y}_1 + \hat{Y}_2 + \dots + \hat{Y}_k + \dots + \hat{Y}_N}$$

# Voltage Division

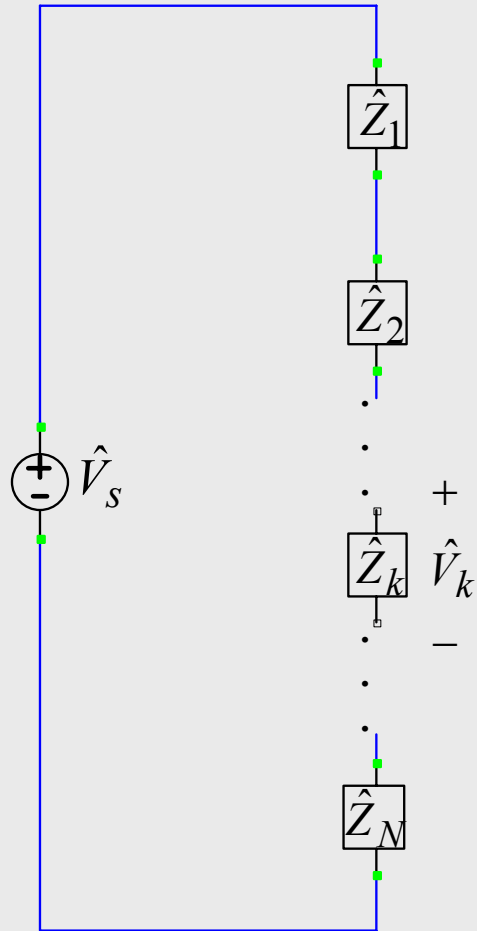

By substituting impedance in for resistance, the voltage division formula can be generalized to:

$$\hat{V}_k = \hat{V}_s \frac{\hat{Z}_k}{\hat{Z}_1 + \hat{Z}_2 + \cdots + \hat{Z}_k + \cdots + \hat{Z}_N}$$

# In-Phase and Out-of-Phase

Voltages and currents are considered *in phase* if the phase angle between their phasor quantities is zero, otherwise they are *out of phase* by an amount equal to their phase difference.

Which quantities are in phase?

$$\hat{V}_1 \angle 45^\circ \quad \hat{V}_2 \angle 0^\circ \quad \hat{V}_2 \angle -90^\circ \quad \hat{I}_1 \angle 270^\circ \quad \hat{I}_2 \angle -45^\circ \quad \hat{I}_2 \angle 45^\circ$$

# Phase Lead and Phase Lab

Out of phase voltages and currents are considered to either lead or lag each other. If the phase of quantity 1 is subtracted from the phase of quantity 2 and the result is positive, then quantity 1 leads quantity 2 or equivalently quantity 2 lags quantity 1.

Given


$$\hat{V}_1 \angle 45^\circ \quad \hat{V}_2 \angle 0^\circ \quad \hat{V}_3 \angle -90^\circ \quad \hat{I}_1 \angle 270^\circ \quad \hat{I}_2 \angle -45^\circ \quad \hat{I}_3 \angle 45^\circ$$

Describe the phase difference between

- $v_1$  and  $i_1$
- $v_2$  and  $i_2$
- $v_3$  and  $i_3$
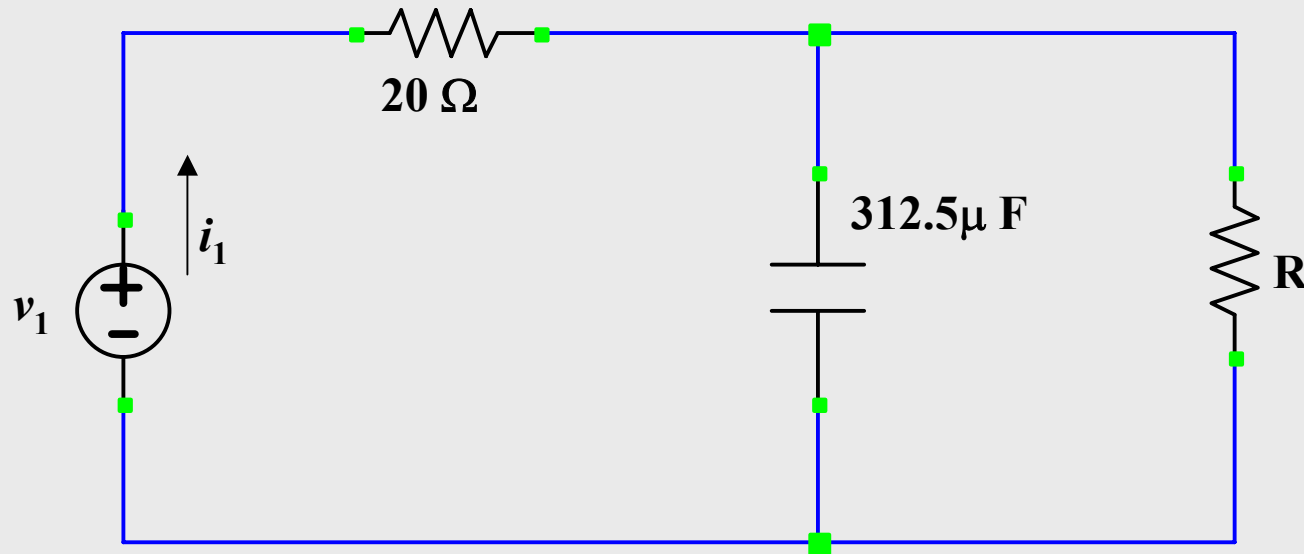
# Example

Find  $R$  such that the  $v_1$  leads  $i_1$  by 15 degrees, if  $v_1 = \cos(400t)$  V



**Show  $R = 15\ \Omega$**