

Phasor Analysis

Phasors, Impedance, SPICE, and Circuit Analysis

Impedance

The conversion of resistive, inductive, and capacitive elements to impedance for a sinusoidal excitation at frequency ω is given by:

$$X_L = \omega L \quad (\text{Reactance})$$

$$X_C = -\frac{1}{\omega C} \quad (\text{Reactance})$$

$$R = R \quad (\text{Resistance})$$

In general impedance is a complex quantity with a resistive component (real) and a reactive component (imaginary):

$$\hat{Z} = R + jX = \sqrt{R^2 + X^2} \angle \tan^{-1}\left(\frac{X}{R}\right)$$

Phasors

Sources can be converted to phasor notation as follows:

$$A \cos(\omega t + \theta) \Leftrightarrow A \angle \theta \qquad A \sin(\omega t + \theta) \Leftrightarrow A \angle \theta - 90^\circ$$


This can be applied to all sources of the same frequency, where ω is used in the impedance conversion of the circuit.

If sources of different frequencies exist, superposition must be applied to solve for a given voltage or current:

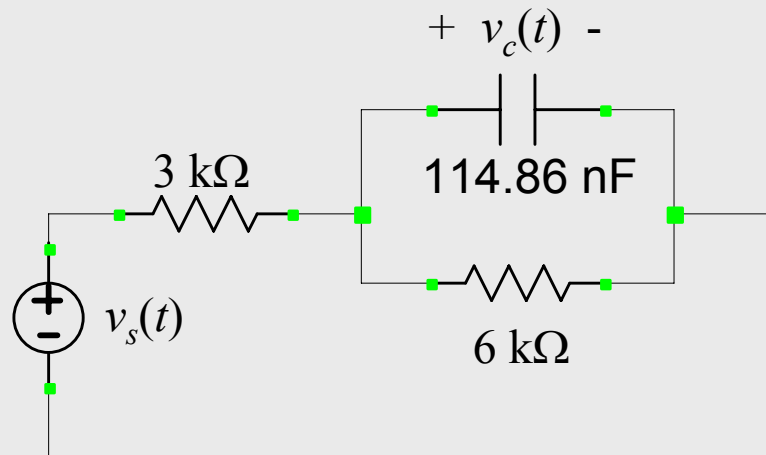- 1. Select sources with a common ω and deactivate all other sources.**
- 2. Convert circuit elements to impedances.**
- 3. Solve for desired voltage or current for selected ω .**
- 4. Repeat steps 1 through 3 for new ω until all sources have been applied.**
- 5. Add together all time-domain solutions obtained in Step 3.**

Loop Analysis Example

Determine the steady-state response for $v_c(t)$ when $v_s(t) = 5\cos(800\pi t)$ V




Show:

$$\hat{V}_c = 2.5000 - j1.4434 = 2.8868 \angle -30^\circ \Leftrightarrow v_c(t) = 2.8868 \cos\left(800\pi t - \frac{\pi}{6}\right) \text{ V}$$

Nodal Analysis Example

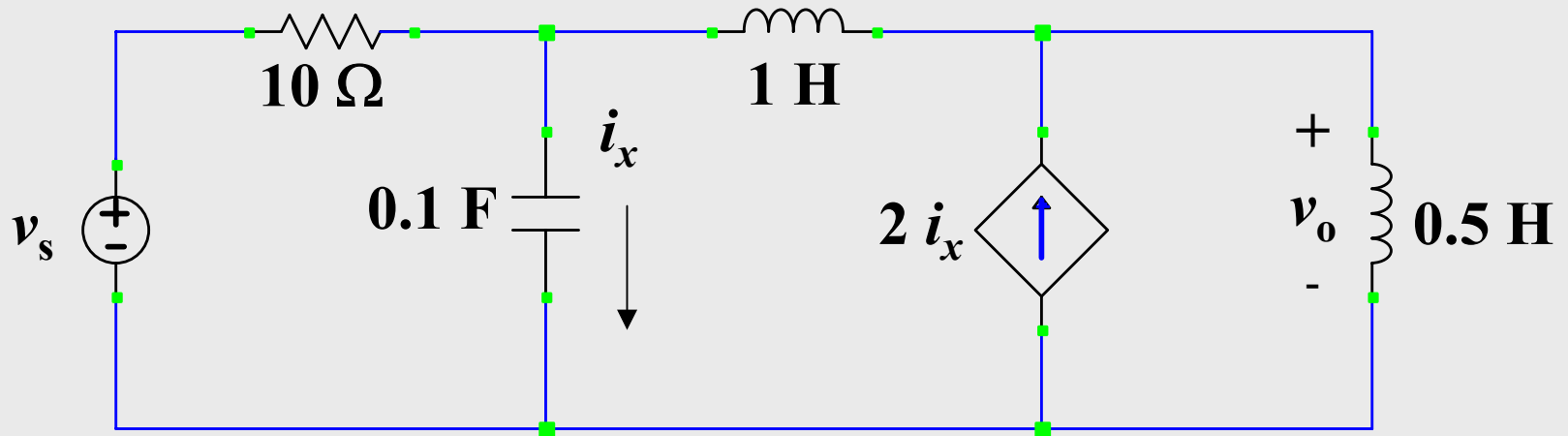
Find the steady-state value of $v_o(t)$ in the circuit below, if $v_s(t) = 20\cos(4t)$:




Show: $v_o(t) = 13.91\cos(4t + 198.3^\circ)$

Multiple Source Example

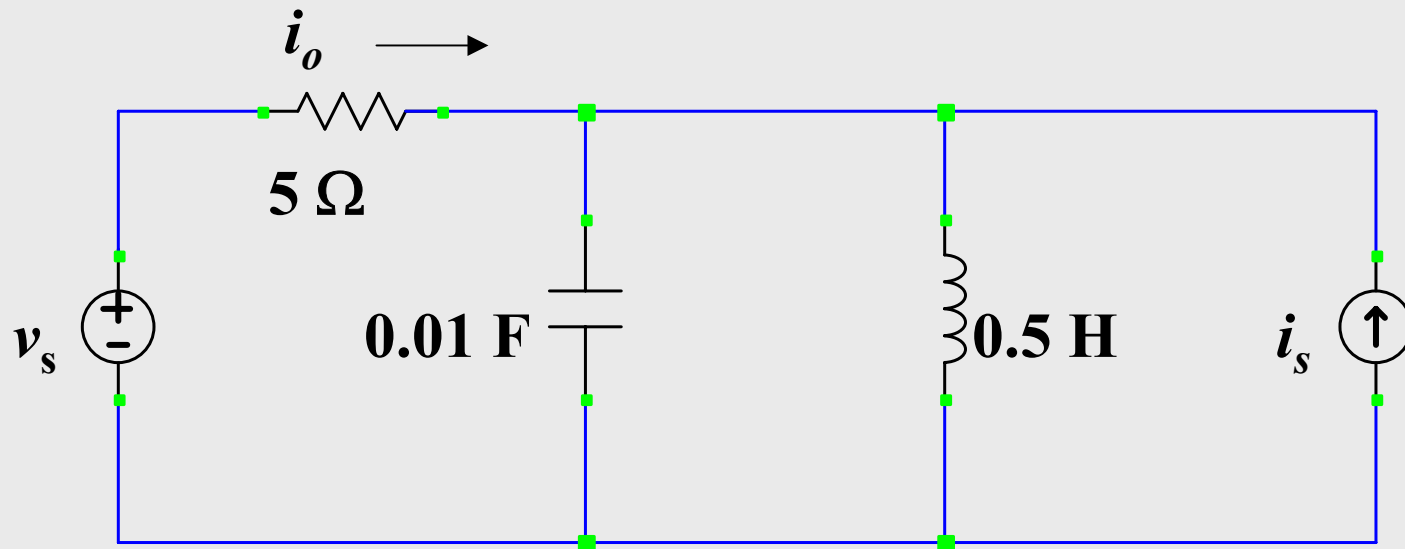Find i_o if $i_s = 3\cos(10t)$ and $v_s = 6\cos(20t + 60^\circ)$




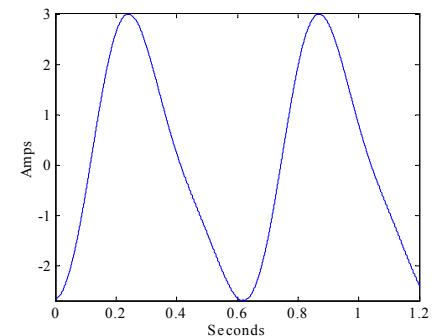Show $i_o = 0.54\cos(20t+123.4^\circ)+2.7\cos(10t-153.4^\circ)$



Equivalent Circuit Example

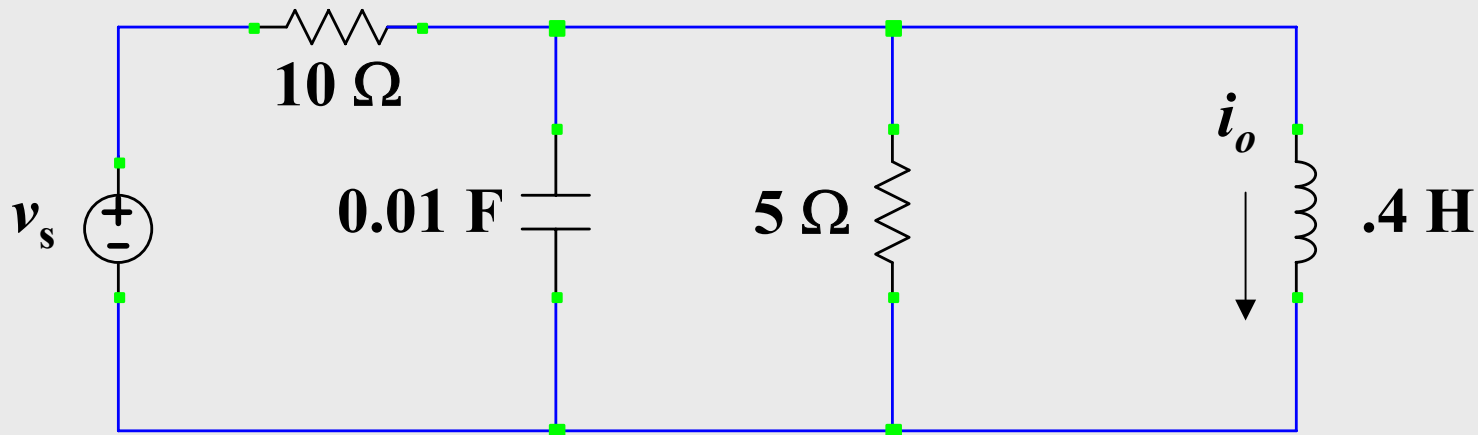
Find i_o steady-state using Norton's Theorem, if $v_s(t) = 2\sin(10t)$:



Show $i_s(t) = .2\sin(10t)$; $Z_{th} = 3 - j = 3.2\angle -18.4^\circ$;
 $i_o = 0.15\cos(10t - 153.4^\circ)$

Equivalent Circuit Example

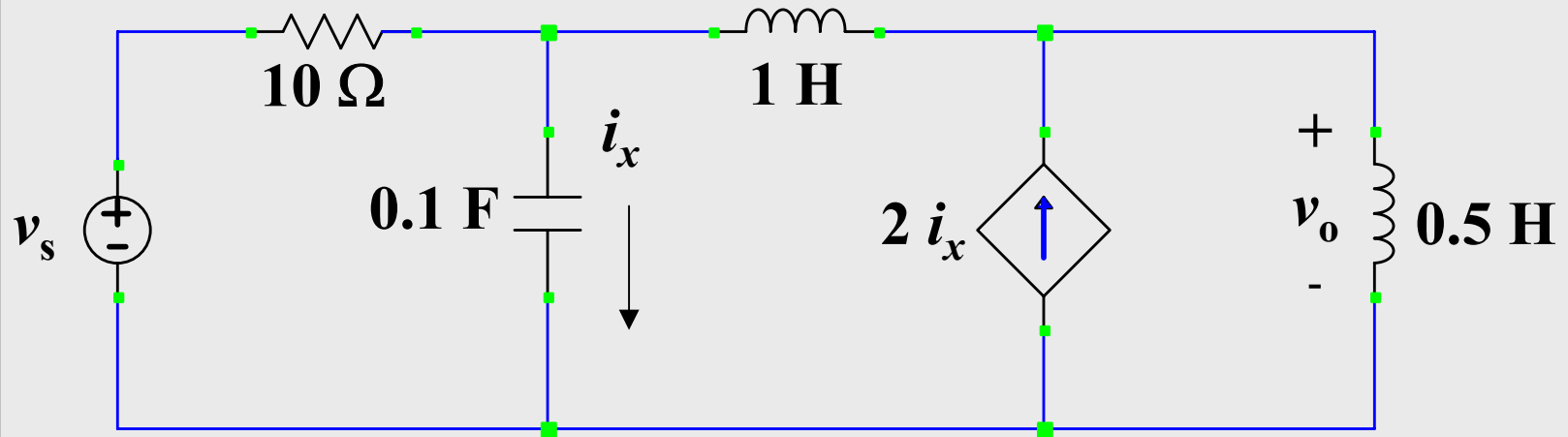Find v_o steady-state using Thévenin's Theorem, if $v_s(t) = 20\cos(4t)$:



$$\hat{I}_{sc} = 6.1 \angle 33.7^\circ$$

$$\hat{V}_{oc} = 10.67 \angle -104^\circ$$

$$\hat{Z}_{th} = 1.75 \angle 137.7^\circ$$

$$v_o(t) = 13.04 \cos(4t - 161.56^\circ)$$