

EE461g: Introduction to Electronic Circuits

Lecture 7


Dr. Lau

University of Kentucky

Outline

- 1 Bipolar Transistor Physics (Sec. 4.1–4.2)
- 2 BJT Output Characteristics (Sec. 4.3)
- 3 Common Emitter Amplifier (Sec. 4.4)
- 4 Operating Regions and Load Line
- 5 Concept of Transconductance (Sec. 4.4.3)
- 6 Small-Signal Model (Sec. 4.4.4)

NPN Bipolar Junction Transistor (BJT)

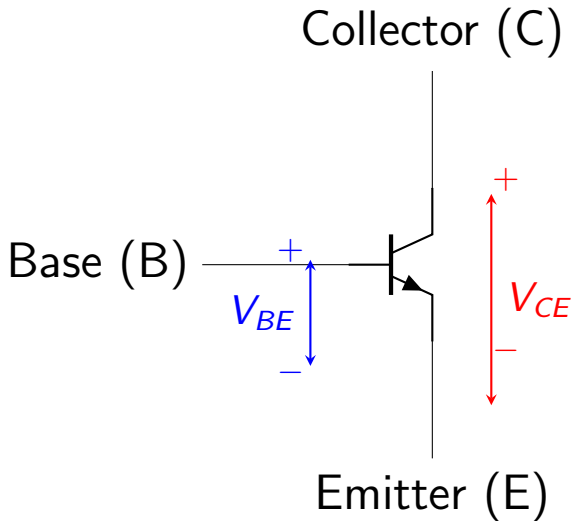

Before continuing with the bipolar transistor, it is instructive to study an interesting effect in pn junctions. Consider the reverse-biased junction depicted in Fig. 4.5(a) and recall from Chapter 2 that the depletion region sustains a strong electric field. Now suppose an electron is somehow “injected” from outside into the right side of the depletion region. What happens to this electron? Serving as a minority carrier on the p side, the electron experiences the electric field and is rapidly swept away into the n side. The ability of a reverse-biased pn junction to efficiently “collect” externally-injected electrons proves essential to the operation of the bipolar transistor.

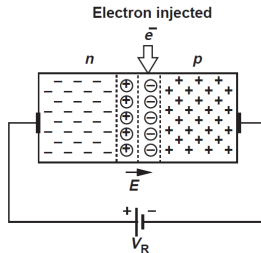


Figure 4.5 Injection of electrons into depletion region.

Source: B. Razavi, *Design of Analog CMOS Integrated Circuits*, 2nd ed., McGraw-Hill, 2017.


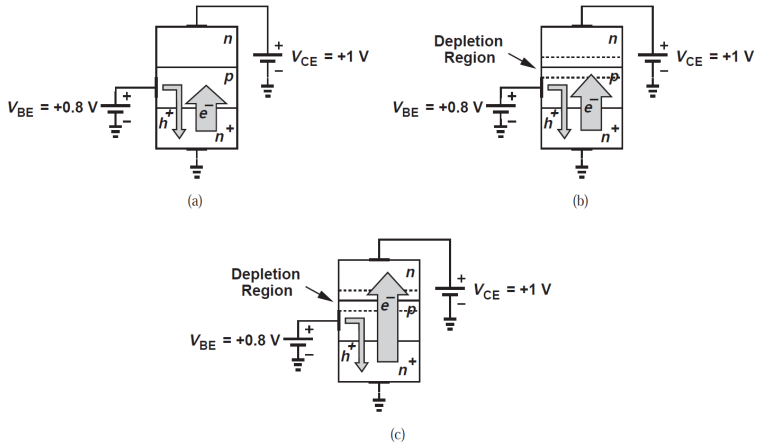



Figure 4.7 (a) Flow of electrons and holes through base-emitter junction, (b) electrons approaching collector junction, (c) electrons passing through collector junction.

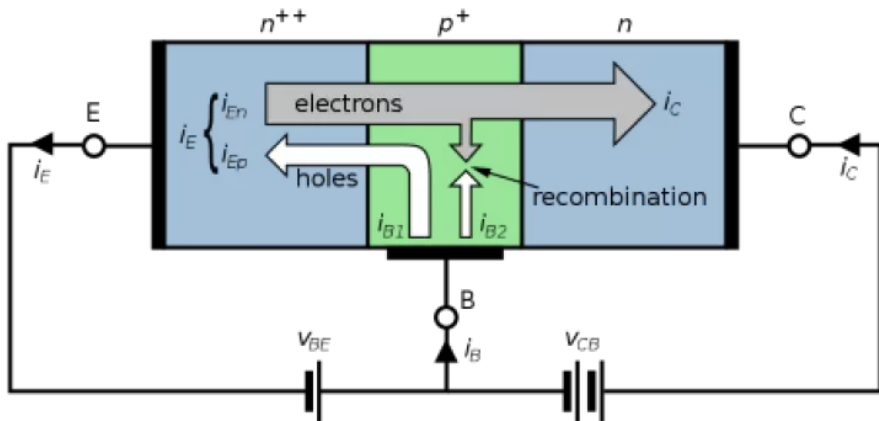Source: B. Razavi, *Design of Analog CMOS Integrated Circuits*, 2nd ed., McGraw-Hill, 2017.





Source: <https://www.emcourse.com/news-blog/bipolar-junction-transistors-what-are-they-what-do-they-do>

BJT Operating Space: V_{BE} vs V_{CE}

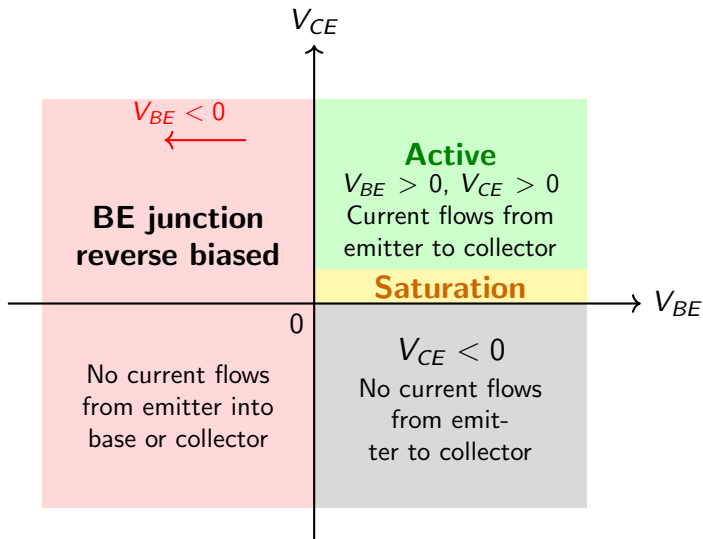


BJT Output Characteristics – Ideal

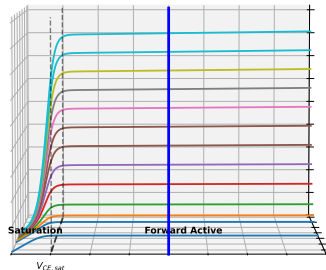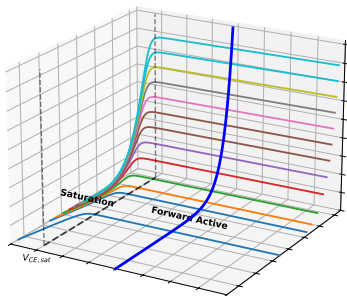


BJT Output Characteristics – Ideal (2D)



BJT Output Characteristics (Ideal)

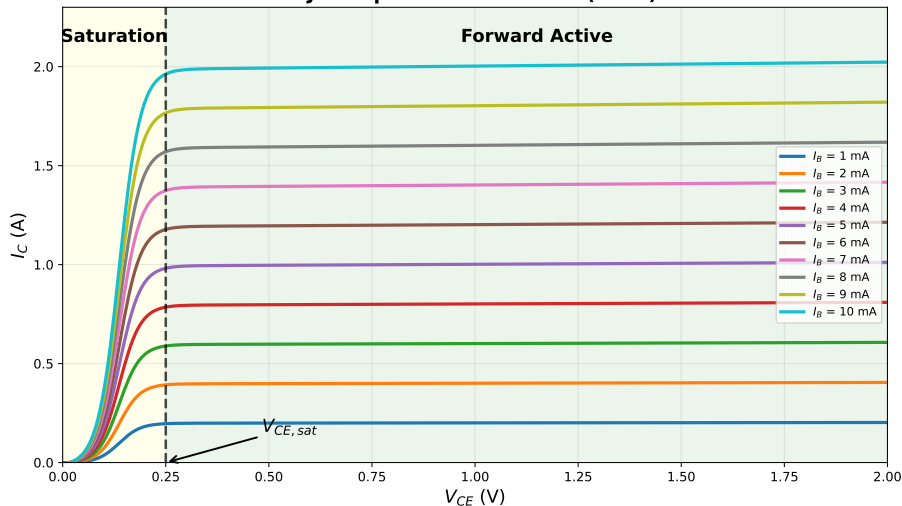

I_C vs V_{BE} at $V_{CE} = 1\text{ V}$

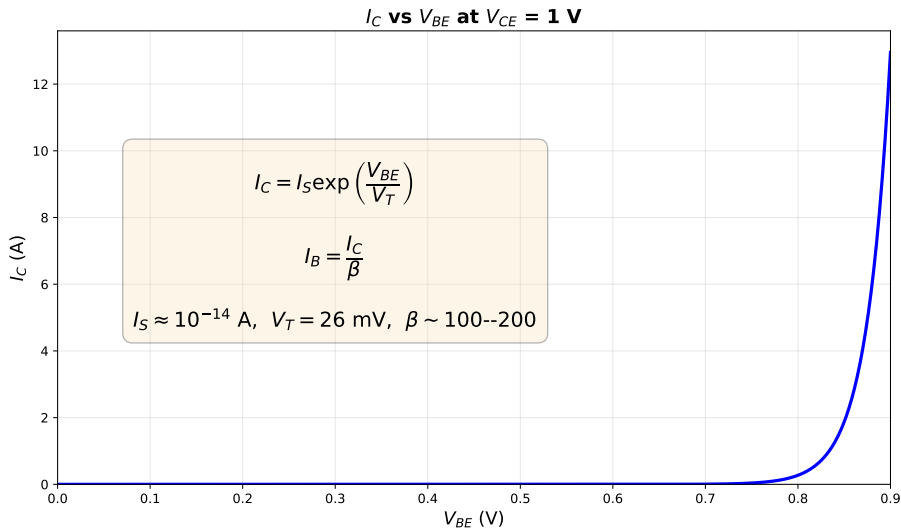


NPN BJT Large-Signal Model

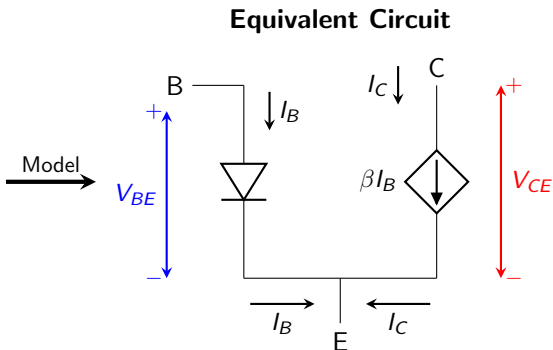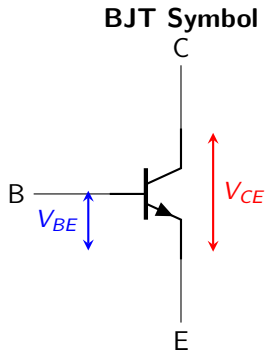

$$I_E = I_B + I_C$$


BJT Output Characteristics (with Early Effect)

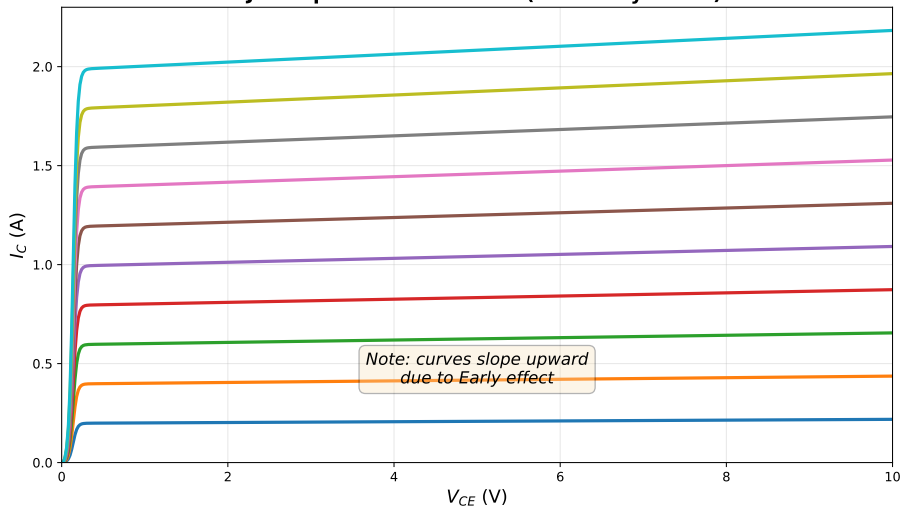BJT Output Characteristics (with Early Effect)




BJT Early Effect – Lines Converge at $-V_A$

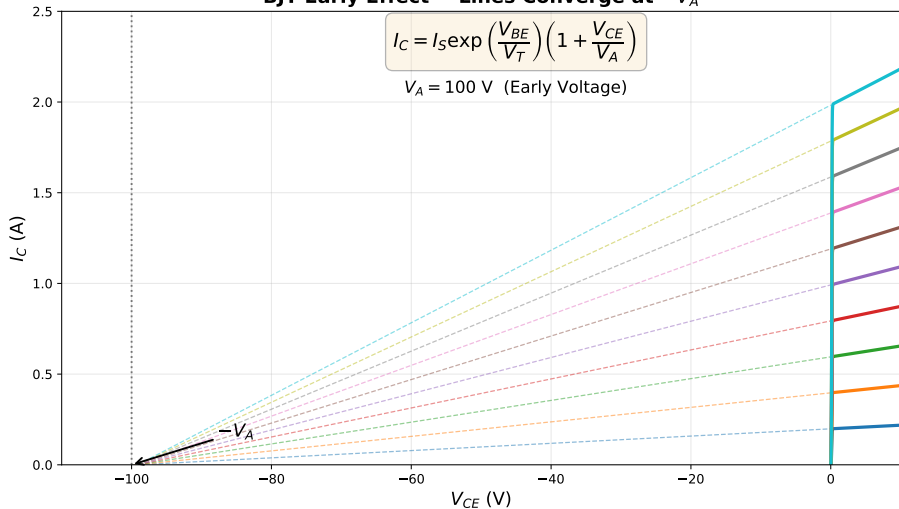BJT Early Effect -- Lines Converge at $-V_A$




BJT Output Characteristics – With Parasitic R

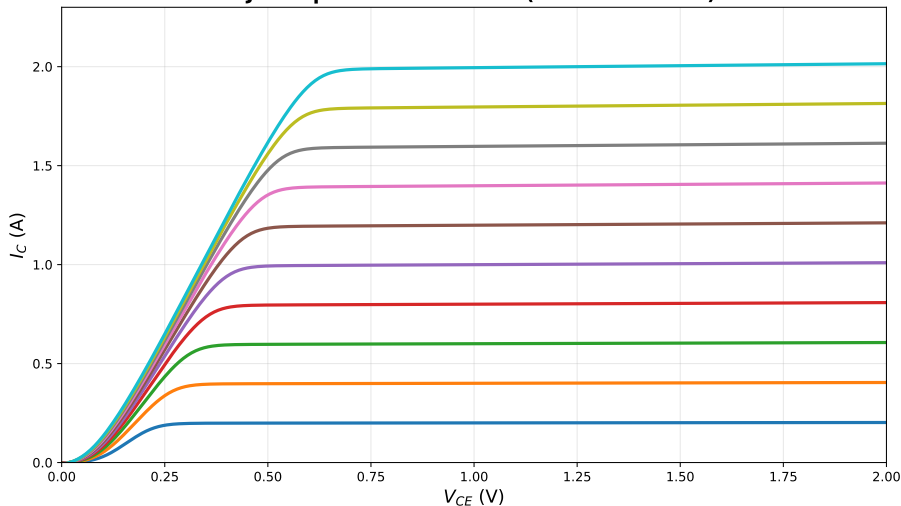BJT Output Characteristics (With Parasitic R)




Common Emitter Amplifier

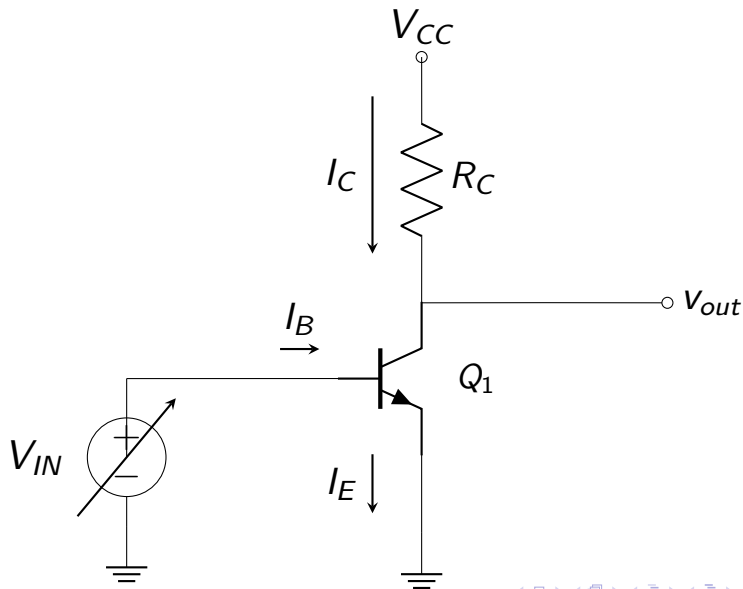

Common Emitter Amplifier – SPICE Simulation

$$V_{CC} = 10 \text{ V} \quad R_C = 100 \, \Omega \quad \beta = 100$$

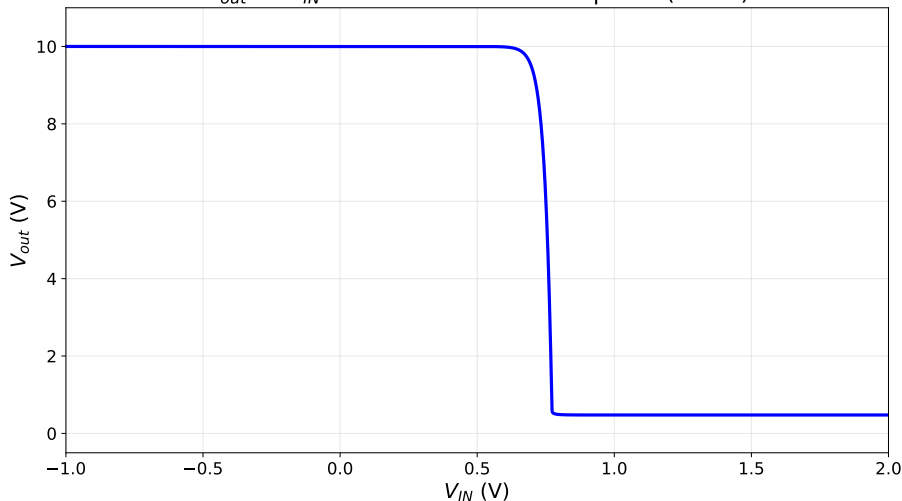V_{out} vs V_{IN} -- Common Emitter Amplifier (SPICE)



Understanding the V_{out} vs V_{IN} Shape

- From the large-signal model and I_C vs V_{BE} relationship:

$$V_{out} = V_{CC} - R_C I_C$$

$$I_C = I_S e^{V_{BE}/V_T}$$


- Since the emitter is grounded: $V_{BE} = V_{IN}$
- As V_{IN} increases, I_C grows exponentially
- V_{out} drops from V_{CC} until the transistor saturates at $V_{CE,sat}$

$$V_{CC} = 10 \text{ V} \quad R_C = 100 \text{ } \Omega \quad \beta = 100$$

Cutoff Region

- $V_{IN} < \sim 0.65 \text{ V}$
- V_{BE} too small to turn on the BJT
- $I_C \approx 0$
- $V_{out} = V_{CC} - R_C \cdot 0 = V_{CC}$

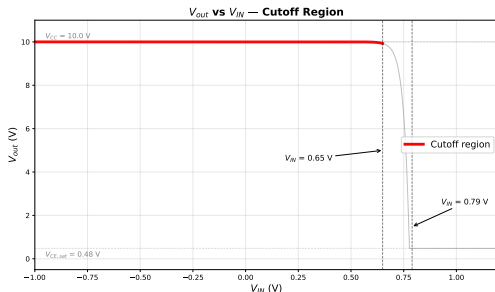
**Output stays flat at V_{CC}
(transistor is OFF)**



Active (Forward-Active) Region


- $V_{IN} \approx 0.65 \text{ V}$ to 0.79 V
- V_{BE} crosses threshold $\Rightarrow I_C$ rises exponentially
- $V_{out} = V_{CC} - R_C I_C$ drops rapidly

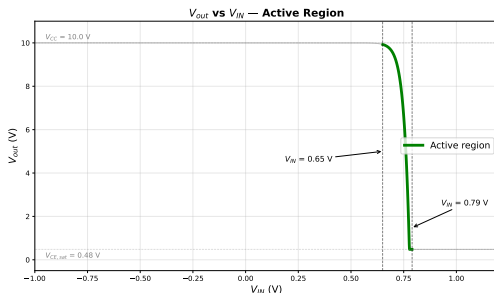Output drops steeply
(high voltage gain region)



Saturation Region

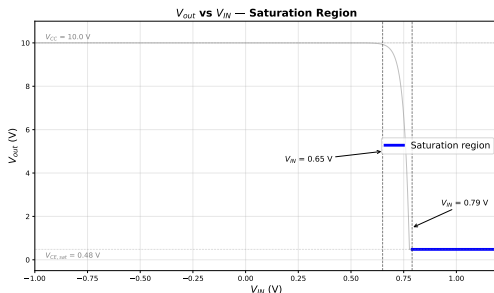- $V_{IN} > \sim 0.79 \text{ V}$
- V_{CE} reaches $V_{CE,sat} \approx 0.48 \text{ V}$
- Collector–base junction forward biases
- I_C can no longer increase freely
- As $V_{IN} \rightarrow \infty$,
 $V_{out} \rightarrow V_{CE,sat} \approx 0 \text{ V}$




Output levels off at $V_{CE,sat}$
(transistor is fully ON)


Load Line Analysis

Load line equation:


$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

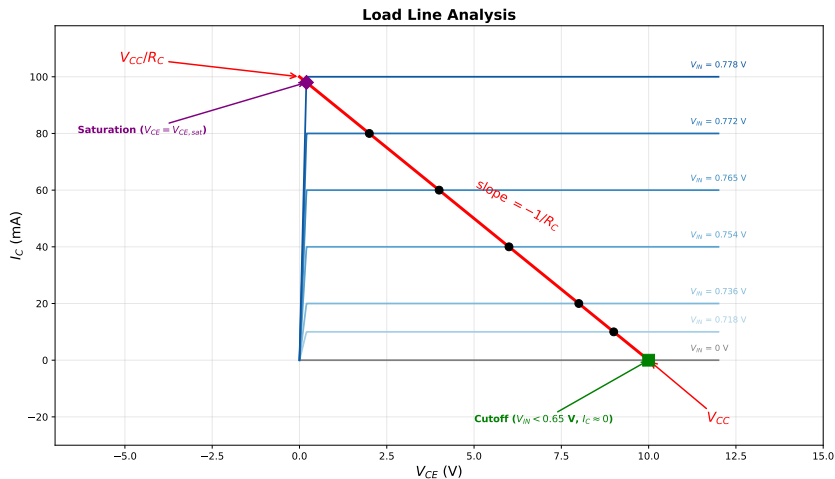

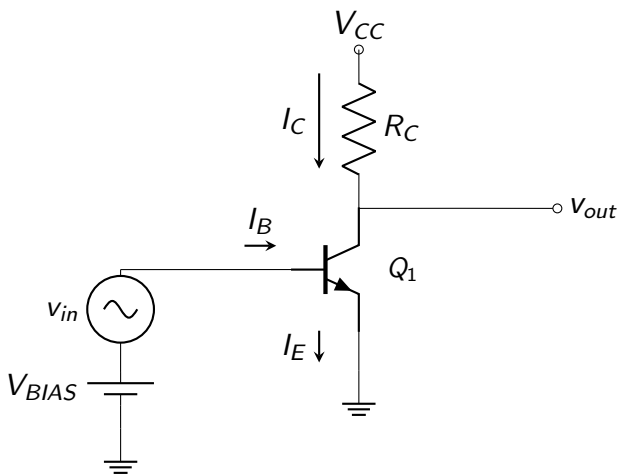
Common Emitter Amplifier with Small-Signal Input



V_{out} vs V_{IN} — Choosing a Q-point

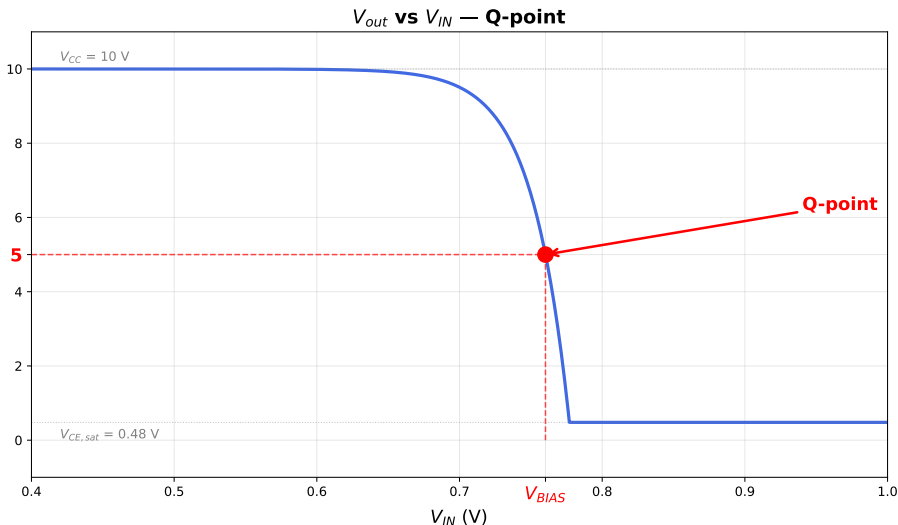

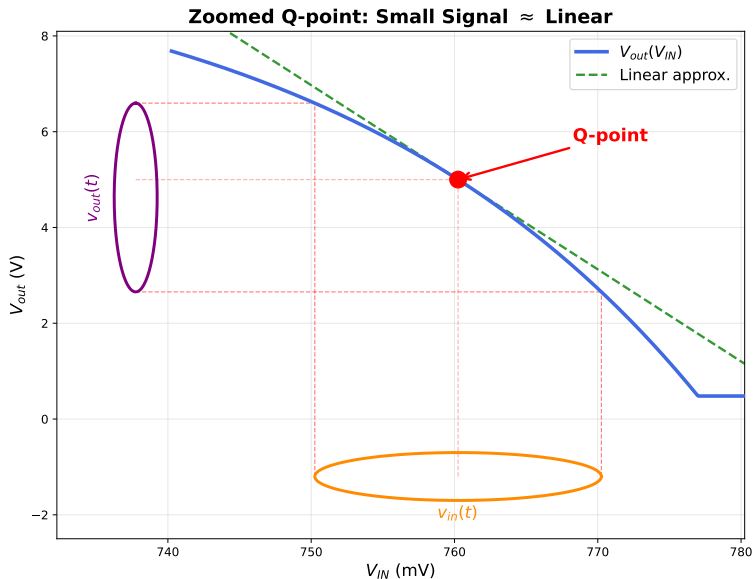Zoomed Q-point: Small Signal $\approx$ Linear




What Happens on the Output Characteristics?

$$V_{out} = V_{CC} - R_C I_C$$

$$I_C = I_S e^{V_{BE}/V_T}$$

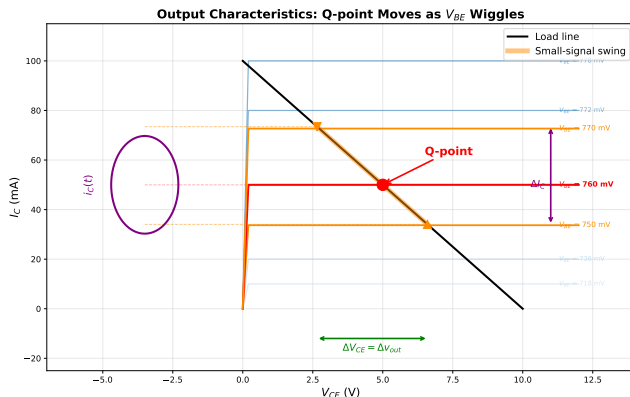As V_{BE} wiggles around V_{BIAS} , I_C changes $\Rightarrow$ Q-point slides along the load line:



From Exponential to Linear: Transconductance g_m

Recall Lecture 1: for the square-law device we linearized I vs V and got a small-signal **resistance** r .


Here: we linearize I_C vs V_{BE} . The slope has units of current / voltage — a **conductance**:

$$g_m = \left. \frac{dI_C}{dV_{BE}} \right|_Q = \frac{I_C}{V_T}$$

We call g_m the **transconductance** because the input voltage (V_{BE}) controls the output current (I_C) — they are at different ports.


g_m tells us: *how much does I_C change for a small change in V_{BE} ?*

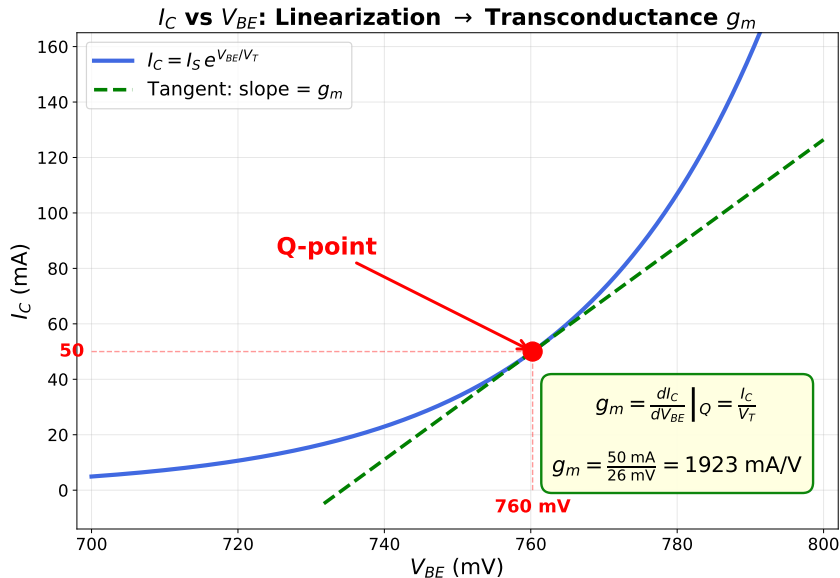I_C vs V_{BE} : Linearization at the Q-point



Small-Signal Equivalent Circuit

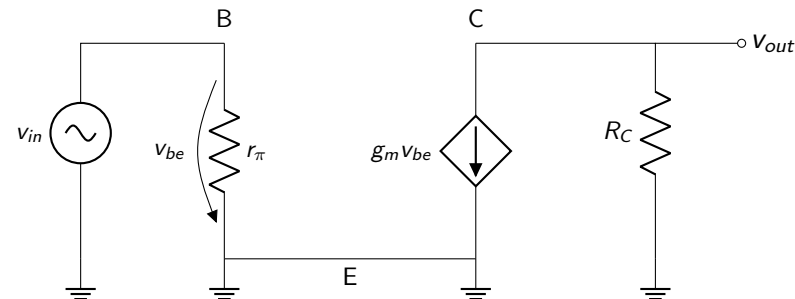Short all DC sources ($V_{BIAS} \rightarrow$ short, $V_{CC} \rightarrow$ short) and replace BJT with small-signal model:



$$v_{be} = v_{in}$$

$$v_{out} = -g_m v_{be} \cdot R_C$$

$$A_v = \frac{v_{out}}{v_{in}} = -g_m R_C$$

Early Effect $\Rightarrow$ Output Resistance r_o


Recall from Lecture 7: with the Early effect, I_C depends on V_{CE} :

$$I_C = I_S e^{V_{BE}/V_T} \left(1 + \frac{V_{CE}}{V_A} \right)$$


The output characteristics are **not perfectly flat** — I_C increases slightly with V_{CE} . This slope is a **conductance** between C and E:

$$\left. \frac{\partial I_C}{\partial V_{CE}} \right|_Q = \frac{I_C}{V_A} \quad \Rightarrow \quad \boxed{r_o = \frac{V_A}{I_C}}$$

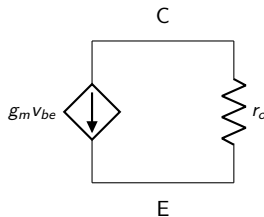Physical meaning: wiggling V_{CE} by a small amount changes I_C a little. This behaves like a **resistor** r_o in parallel with the current source $g_m v_{be}$.



Complete Small-Signal Model of the BJT

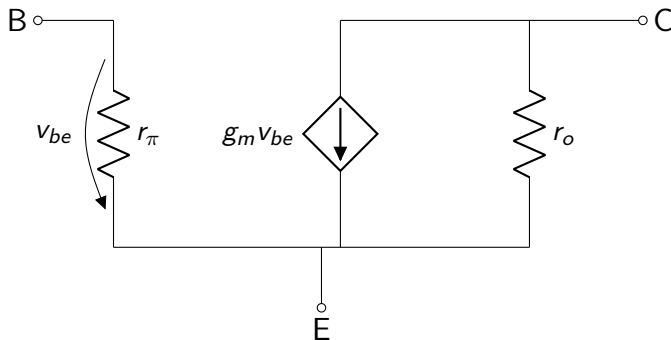

$$g_m = \frac{I_C}{V_T}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{\beta V_T}{I_C}$$

$$r_o = \frac{V_A}{I_C}$$