

EE461g: Introduction to Electronic Circuits

Lecture 12

Dr. Lau


University of Kentucky

Outline

- 1 The CE Amplifier Circuit
- 2 CE Large-Signal Analysis (DC Bias)
- 3 CE Small-Signal Analysis (AC Gain)
- 4 The CS Amplifier Circuit
- 5 CS Large-Signal Analysis (DC Bias)
- 6 CS Small-Signal Analysis (AC Gain)
- 7 Two-Port Network Model
- 8 BJT vs MOSFET Comparison
- 9 SPICE Verification

The CE Amplifier Circuit

 
The CE Amplifier with Voltage Divider Bias



CE Large-Signal Analysis (DC Bias)

Capacitors as Open Circuits at DC

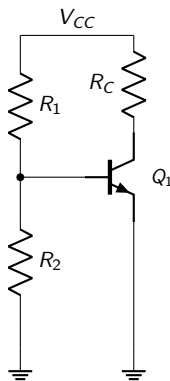- For **DC analysis**, coupling capacitors (C_{in} , C_{out}) are **open circuits**
- Large capacitors block DC current: $I_C = C \cdot dV/dt = 0$ at DC
- This **disconnects** v_{in} , R_{in} , and R_L from the circuit
- Only the bias network (R_1 , R_2) and R_C remain



Key idea: At DC, the amplifier reduces to a simple bias circuit

Thévenin Equivalent of the Bias Network


Step 1: Remove Q_1 from the base node.

Step 2: Open-circuit voltage (voltage divider):

$$V_{BIAS} = V_{CC} \cdot \frac{R_2}{R_1 + R_2}$$

Step 3: Short V_{CC} , find resistance:
 
$$R_{TH} = R_1 \parallel R_2 = \frac{R_1 \cdot R_2}{R_1 + R_2}$$



Finding the Q-Point

KVL around the base-emitter loop:

$$V_{BIAS} = I_B \cdot R_{TH} + V_{BE}$$

Since $I_C = \beta I_B$, substitute $I_B = I_C/\beta$:

$$V_{BIAS} = \frac{I_C}{\beta} \cdot R_{TH} + V_{BE}$$

Problem: V_{BE} depends on I_C (exponential relationship), so we must solve **iteratively** (as in Lectures 7–8)

Iterative approach:

- 1 Guess $V_{BE} \approx 0.7 \text{ V} \Rightarrow$ solve for I_C
- 2 Update V_{BE} using $V_{BE} = V_T \ln(I_C/I_S)$
- 3 Repeat until V_{BE} converges

Collector-emitter voltage:

$$V_{CE} = V_{CC} - I_C \cdot R_C$$

CE Amplifier Q-Point

$$I_C = \frac{\beta (V_{BIAS} - V_{BE})}{R_{TH}}$$

$$V_{CE} = V_{CC} - I_C \cdot R_C$$

$$V_{BIAS} = V_{CC} \cdot \frac{R_2}{R_1 + R_2}$$

Verify: $V_{CE} > V_{BE}$ to confirm the transistor is in **forward active** mode

CE Small-Signal Analysis (AC Gain)

Capacitors as Short Circuits at AC

- For **AC small-signal analysis**, coupling capacitors are **short circuits**
- At signal frequencies: $Z_C = 1/(j\omega C) \approx 0$ for large C
- DC voltage sources (V_{CC}) are also **shorted to ground**

Result: C_{in} connects v_{in} directly to the base network; C_{out} connects R_L directly to the collector


Small-signal model parameters (from Q-point):

$$g_m = \frac{I_C}{V_T}$$

$$r_\pi = \frac{\beta}{g_m}$$

$$r_o = \frac{V_A}{I_C}$$

CE Small-Signal Equivalent Circuit

 

$R_1 \parallel R_2$ at input, r_{π} from base to emitter, $g_m v_{be}$ controlled source, $r_o \parallel R_C \parallel R_L$ at output

CE Voltage Gain Derivation

Step 1: Input voltage divider determines v_{be} :

$$v_{be} = v_{in} \cdot \frac{R_1 \parallel R_2 \parallel r_{\pi}}{R_{in} + R_1 \parallel R_2 \parallel r_{\pi}}$$

Step 2: Output voltage from controlled source:

$$v_{out} = -g_m v_{be} \cdot (r_o \parallel R_C \parallel R_L)$$

Step 3: Overall voltage gain:

$$A_v = \frac{v_{out}}{v_{in}} = -g_m \cdot \frac{R_1 \parallel R_2 \parallel r_{\pi}}{R_{in} + R_1 \parallel R_2 \parallel r_{\pi}} \cdot (r_o \parallel R_C \parallel R_L)$$

Negative sign $\Rightarrow$ CE amplifier is **inverting**

CE Gain — Simplified

If $R_1 \parallel R_2 \gg r_\pi$ (typical for well-designed bias):

$$R_1 \parallel R_2 \parallel r_\pi \approx r_\pi$$

Simplified voltage gain:

$$A_v \approx -g_m \cdot \frac{r_\pi}{R_{in} + r_\pi} \cdot (R_C \parallel R_L)$$


If additionally $r_o \gg R_C \parallel R_L$ (often true):

$$r_o \parallel R_C \parallel R_L \approx R_C \parallel R_L$$

The gain is set by g_m , the input voltage divider (r_π vs R_{in}), and the output parallel resistance ($R_C \parallel R_L$)

The CS Amplifier Circuit

 The CS Amplifier with Voltage Divider Bias




CS Large-Signal Analysis (DC Bias)

Capacitors as Open Circuits at DC

- Same principle: C_{in} and C_{out} are open circuits at DC
- Disconnects v_{in} , R_{in} , and R_L
- Only bias network (R_1 , R_2) and R_D remain

 Key difference: $I_G = 0$ for a MOSFET, so R_{TH} has **no effect** on the gate voltage!



Thévenin Equivalent of the Bias Network

Same Thévenin procedure:


$$V_{BIAS} = V_{DD} \cdot \frac{R_2}{R_1 + R_2}$$

$$R_{TH} = R_1 \parallel R_2$$

Since $I_G = 0$:

$$V_{GS} = V_{BIAS} - I_G \cdot R_{TH} = V_{BIAS}$$

No voltage drop across R_{TH} !

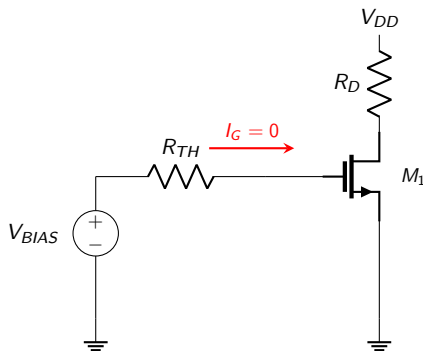

Finding the Q-Point

Since $I_G = 0$:

$$V_{GS} = V_{BIAS} = V_{DD} \cdot \frac{R_2}{R_1 + R_2}$$

Drain current (saturation region):

$$I_{DS} = \frac{K_n}{2} (V_{GS} - V_{TN})^2$$

Drain-source voltage:

$$V_{DS} = V_{DD} - I_{DS} \cdot R_D$$

No iteration needed! Unlike the BJT, V_{GS} is known directly from the voltage divider. Just plug in and solve.

CS Amplifier Q-Point

$$V_{GS} = V_{DD} \cdot \frac{R_2}{R_1 + R_2}$$

$$I_{DS} = \frac{K_n}{2} (V_{GS} - V_{TN})^2$$

$$V_{DS} = V_{DD} - I_{DS} \cdot R_D$$

Verify: $V_{DS} > V_{GS} - V_{TN}$ to confirm the MOSFET is in **saturation**

CS Small-Signal Analysis (AC Gain)

Capacitors as Short Circuits at AC

- Same principle as BJT case: capacitors become short circuits at AC
- DC source V_{DD} is shorted to ground
- C_{in} connects v_{in} directly to the gate network
- C_{out} connects R_L directly to the drain


Small-signal model parameters (from Q-point):

$$g_m = K_n (V_{GS} - V_{TN})$$

$$r_o = \frac{1}{\lambda I_{DS}}$$

No r_{π} ! The MOSFET gate draws zero current $\Rightarrow$ infinite input impedance

CS Small-Signal Equivalent Circuit

 

$R_1 \parallel R_2$ at input, gate is open (no r_{π}), $g_m v_{gs}$ controlled source, $r_o \parallel R_D \parallel R_L$ at output

CS Voltage Gain Derivation

Step 1: Input voltage divider determines v_{gs} :

$$v_{gs} = v_{in} \cdot \frac{R_1 \parallel R_2}{R_{in} + R_1 \parallel R_2}$$

No r_{π} in parallel! The gate is an open circuit, so only $R_1 \parallel R_2$ loads the input.

Step 2: Output voltage:

$$v_{out} = -g_m v_{gs} \cdot (r_o \parallel R_D \parallel R_L)$$

Step 3: Overall voltage gain:

$$A_v = \frac{v_{out}}{v_{in}} = -g_m \cdot \frac{R_1 \parallel R_2}{R_{in} + R_1 \parallel R_2} \cdot (r_o \parallel R_D \parallel R_L)$$


CS Amplifier Voltage Gain

$$A_v = -g_m \cdot \frac{R_1 \parallel R_2}{R_{in} + R_1 \parallel R_2} \cdot (r_o \parallel R_D \parallel R_L)$$

- **Simpler** than the BJT CE gain — no r_π term in the input divider
- Infinite gate impedance means $R_1 \parallel R_2$ can be made very large without loss
- Still **inverting** (negative sign)


Two-Port Network Model

What is a Two-Port Network?

 

- A **two-port network** is a “black box” with an input port and an output port
- For a **voltage amplifier**, fully characterized by three parameters:
 - ① **Input impedance** Z_{in} : resistance looking into the input
 - ② **Output impedance** Z_{out} : resistance looking back into the output
 - ③ **Open-circuit voltage gain** A_{vo} : gain when $R_L = \infty$
- Our small-signal amplifier models *are* two-port networks

Voltage Amplifier Two-Port Equivalent

 

The overall voltage gain is a product of **three factors**:

$$A_v = \frac{v_o}{v_s} = \underbrace{\frac{Z_{in}}{R_{in} + Z_{in}}}_{\text{input divider}} \cdot A_{vo} \cdot \underbrace{\frac{R_L}{Z_{out} + R_L}}_{\text{output divider}}$$


Once you know Z_{in} , Z_{out} , and A_{vo} , you can find the gain for **any** source and load

Deriving the Input Impedance Z_{in}

Method: Disconnect the source. Look into the input port of the small-signal circuit.


DC supplies are **AC ground**; capacitors are **short circuits**.

CE (BJT)

 

$$Z_{in} = R_1 \parallel R_2 \parallel r_{\pi}$$

CS (MOSFET)

 

$$Z_{in} = R_1 \parallel R_2$$


The MOSFET's infinite gate impedance means r_{π} does **not** load the input $\Rightarrow$ CS has higher Z_{in} than CE

Deriving Z_{out} and A_{vo}

Z_{out} : Zero the input ($v_{be} = 0$ or $v_{gs} = 0$), so $g_m \cdot 0 = 0$ — controlled source turns off.


Look back into the output port.

CE (BJT)

 

$$Z_{out} = r_o \parallel R_C$$

CS (MOSFET)

 

$$Z_{out} = r_o \parallel R_D$$

A_{vo} (open-circuit gain): Set $R_L = \infty$. Since $v_{be} = v_i$ (or $v_{gs} = v_i$):

$$v_o = -g_m v_i \cdot Z_{out} \Rightarrow A_{vo} = -g_m \cdot Z_{out}$$

CE and CS Two-Port Parameters

Parameter	CE (BJT)	CS (MOSFET)
Z_{in}	$R_1 \parallel R_2 \parallel r_{\pi}$	$R_1 \parallel R_2$
Z_{out}	$r_o \parallel R_C$	$r_o \parallel R_D$
A_{vo}	$-g_m (r_o \parallel R_C)$	$-g_m (r_o \parallel R_D)$

Key difference: The MOSFET gate draws no current $\Rightarrow$ no r_{π} loading the input

CS amplifier has **higher input impedance** than CE

Finding Z_{out} : Zero the input ($v_{be} = 0$ or $v_{gs} = 0$), short DC supplies to ground,

and find the resistance looking back into the output node

BJT vs MOSFET Comparison

CE vs CS Amplifier — Side-by-Side

Property	BJT (CE)	MOSFET (CS)
Bias voltage	$V_{BIAS} = V_{CC} \frac{R_2}{R_1 + R_2}$	$V_{BIAS} = V_{DD} \frac{R_2}{R_1 + R_2}$
Effect of R_{TH}	Drops voltage ($I_B \neq 0$)	No effect ($I_G = 0$)
Q-point method	Iterative (exponential)	Direct (square-law)
Input impedance	$R_1 \parallel R_2 \parallel r_\pi$	$R_1 \parallel R_2$ (infinite gate)
Input divider	$\frac{R_1 \parallel R_2 \parallel r_\pi}{R_{in} + R_1 \parallel R_2 \parallel r_\pi}$	$\frac{R_1 \parallel R_2}{R_{in} + R_1 \parallel R_2}$
Gain	$-g_m \cdot (\text{div}) \cdot (r_o \parallel R_C \parallel R_L)$	$-g_m \cdot (\text{div}) \cdot (r_o \parallel R_D \parallel R_L)$

Same structure, but the MOSFET's infinite gate impedance simplifies both bias and gain analysis

SPICE Verification


CE SPICE Verification — Q-Point

```
* CE Amplifier - Operating Point
.options TEMP=28.42 TNOM=28.42
VCC vcc 0 DC 10
R1 vcc base 200k
R2 base 0 100k
Q1 col base 0 NPN1
RC vcc col 1k
.model NPN1 NPN(IS=1e-14
+ BF=100)
.end
```

	Analytical	SPICE	
I_C	3.96 mA	3.96 mA	✓
V_{BE}	0.694 V	0.694 V	✓
V_{CE}	6.04 V	6.04 V	✓

SPICE confirms our iterative Q-point solution — values match exactly

CE SPICE Verification — Voltage Gain

 

	Analytical	SPICE
A_v	-54.6	-54.6


CS SPICE Verification — Q-Point

```
* CS Amplifier - Operating Point
VDD vdd 0 DC 10
R1 vdd gate 400k
R2 gate 0 100k
M1 drain gate 0 0 NMOS1
+ W=1u L=1u
RD vdd drain 1k
.model NMOS1 NMOS(KP=8m
+ VTO=1 LAMBDA=0)
.end
```

	Analytical	SPICE	
I_{DS}	4.00 mA	4.00 mA	✓
V_{GS}	2.00 V	2.00 V	✓
V_{DS}	6.00 V	6.00 V	✓

SPICE confirms the direct Q-point calculation — values match exactly

CS SPICE Verification — Voltage Gain

 

	Analytical	SPICE
A_v	-7.2	-7.2

SPICE Verification — Summary

All analytical results confirmed by SPICE — exact match for Q-point and gain

Numerical Two-Port Parameters from SPICE Circuits

Parameter	CE (BJT)	CS (MOSFET)
g_m	152.4 mA/V	8.0 mA/V
r_π	657 Ω	∞
r_o	∞ (no V_A)	∞ ($\lambda = 0$)
Z_{in}	$R_1 \parallel R_2 \parallel r_\pi = 650 \Omega$	$R_1 \parallel R_2 = 80 \text{ k}\Omega$
Z_{out}	$r_o \parallel R_C = 1.00 \text{ k}\Omega$	$r_o \parallel R_D = 1.00 \text{ k}\Omega$
A_{vo}	-152.4	-8.0
A_v	-54.6	-7.2

CE has much higher g_m (and $|A_{vo}|$), but its low Z_{in} causes significant input signal loss