

EE461g: Introduction to Electronic Circuits

Lecture 18

Dr. Lau

University of Kentucky


Outline

- 1 NMOS with Current Source Biasing
- 2 Finding the Source Voltage V_S
- 3 Finding the Drain Voltage V_D
- 4 Verifying Saturation
- 5 Maximum V_{BIAS} for Saturation
- 6 Summary
- 7 MOSFET Current Mirror Implementation
- 8 Minimum V_{BIAS} for M_4 Saturation
- 9 The Differential Pair
- 10 BJT Differential Pair
- 11 Summary

NMOS Biasing

with a Current Source

The Circuit

 

Circuit description:

$+V_{DD}$ supplies current through R_D to the drain

Gate is held at a fixed DC voltage V_{BIAS}

A current source I_{REF} is connected from the source to $-V_{DD}$

The current source **fixes** $I_D = I_{REF}$

Goal: Find V_D and V_S

Finding V_S

The Source Voltage

Step 1: Assume Saturation

We assume M_1 operates in **saturation**. We will verify this at the end.

In saturation, the drain current is:

$$I_D = \frac{k'_n}{2} \left(\frac{W}{L} \right) (V_{GS} - V_{TN})^2$$

Since the current source fixes $I_D = I_{REF}$:

$$I_{REF} = \frac{k'_n}{2} \left(\frac{W}{L} \right) (V_{GS} - V_{TN})^2$$

The current is **known**. We can solve this equation for V_{GS} .

Step 2: Solve for V_{GS}

Starting from: $I_{REF} = \frac{k'_n}{2} \left(\frac{W}{L} \right) (V_{GS} - V_{TN})^2$

Isolate the squared term: $(V_{GS} - V_{TN})^2 = \frac{2I_{REF}}{k'_n(W/L)}$

Take the square root (positive root since $V_{GS} > V_{TN}$ in saturation):

$$V_{GS} - V_{TN} = \sqrt{\frac{2I_{REF}}{k'_n(W/L)}}$$

$$V_{GS} = V_{TN} + \sqrt{\frac{2I_{REF}}{k'_n(W/L)}}$$

V_{GS} depends only on the current I_{REF} , transistor parameters, and V_{TN} .

Step 3: Extract V_S from V_{GS}

By definition:

$$V_{GS} = V_G - V_S$$

Since $V_G = V_{BIAS}$:

$$V_S = V_G - V_{GS} = V_{BIAS} - V_{GS}$$

Substituting our expression for V_{GS} :

$$V_S = V_{BIAS} - V_{TN} - \sqrt{\frac{2I_{REF}}{k'_n(W/L)}}$$

V_S is completely determined by V_{BIAS} , the current source I_{REF} , and transistor parameters.

Finding V_D

The Drain Voltage

Step 4: Apply KVL Through R_D

The current through R_D is $I_D = I_{REF}$ (set by the current source I_{REF}).

Applying KVL from $+V_{DD}$ through R_D to the drain:

$$V_D = V_{DD} - I_D \cdot R_D$$

Since $I_D = I_{REF}$:

$$V_D = V_{DD} - I_{REF} \cdot R_D$$

V_D depends only on V_{DD} , the current I_{REF} , and R_D . It does not depend on transistor parameters!

Verifying Saturation Condition

Step 5: Check the Saturation Condition

For an NMOS in saturation, we need:

$$V_{DS} \geq V_{GS} - V_{TN} \quad (\text{equivalently, } V_D \geq V_G - V_{TN})$$

We can compute V_{DS} :

$$V_{DS} = V_D - V_S = (V_{DD} - I_{REF}R_D) - \left(V_{BIAS} - V_{TN} - \sqrt{\frac{2I_{REF}}{k'_n(W/L)}} \right)$$

And the overdrive voltage is:

$$V_{OV} = V_{GS} - V_{TN} = \sqrt{\frac{2I_{REF}}{k'_n(W/L)}}$$

Check: $V_{DS} \geq V_{OV}$. If yes, our saturation assumption is valid.

Maximum V_{BIAS}

Keeping the MOSFET in Saturation

Step 6: Set Up the Saturation Inequality

The saturation condition requires:

$$V_{DS} \geq V_{GS} - V_{TN}$$

Rewrite using $V_{DS} = V_D - V_S$:

$$V_D - V_S \geq V_{GS} - V_{TN}$$

Since $V_{GS} = V_G - V_S = V_{BIAS} - V_S$, substituting:

$$V_D - V_S \geq V_{BIAS} - V_S - V_{TN}$$

The V_S terms cancel:

$$V_D \geq V_{BIAS} - V_{TN}$$

The saturation condition simplifies to a constraint on V_D and V_{BIAS} only.

Step 7: Substitute V_D and Solve for V_{BIAS}

Substitute $V_D = V_{DD} - I_{REF} \cdot R_D$:

$$V_{DD} - I_{REF} \cdot R_D \geq V_{BIAS} - V_{TN}$$

Rearrange to isolate V_{BIAS} :

$$V_{BIAS} \leq V_{DD} - I_{REF} \cdot R_D + V_{TN}$$

Therefore the maximum value of V_{BIAS} is:

$$V_{BIAS, \max} = V_{DD} - I_{REF} \cdot R_D + V_{TN}$$

If V_{BIAS} exceeds this value, the MOSFET enters the **triode** (linear) region and the current source can no longer set $I_D = I_{REF}$.

$$V_{BIAS,max} = \underbrace{V_{DD} - I_{REF} \cdot R_D}_{V_D} + V_{TN}$$

$V_{BIAS,max}$ equals the drain voltage plus one threshold voltage


Increasing V_{BIAS} beyond this pushes $V_{GS} - V_{TN}$ above V_{DS} — the transistor leaves saturation

Larger R_D $\rightarrow$ larger voltage drop $\rightarrow$ lower $V_D \rightarrow$ lower $V_{BIAS,max}$

Larger I_{REF} $\rightarrow$ same effect: lower $V_D \rightarrow$ lower $V_{BIAS,max}$

Design trade-off: A larger R_D gives more voltage gain but restricts the allowable range of V_{BIAS} .

Summary of Results

 

Source voltage:

$$V_S = V_{BIAS} - V_{TN} - \sqrt{\frac{2I_{REF}}{k'_n(W/L)}}$$

Drain voltage:

$$V_D = V_{DD} - I_{REF} \cdot R_D$$

Max V_{BIAS} for saturation:


$$V_{BIAS,max} = V_{DD} - I_{REF} \cdot R_D + V_{TN}$$

The current source makes I_D independent of V_{BIAS} drift — but V_{BIAS} must stay below $V_{BIAS,max}$.

Replacing the Ideal Current Source

PMOS + NMOS Current Mirror from Lecture
16

The Complete Circuit

 

Left side (bias network):

M_2 (PMOS, diode-connected), R_{REF} , and M_3 (NMOS, diode-connected) set I_{REF}

$$I_{REF} = \frac{2V_{DD} - |V_{GS2}| - V_{GS3}}{R_{REF}}$$

Right side:

M_4 mirrors I_{REF} from M_3 (same V_{GS})

$$\text{Current ratio: } I_D = I_{REF} \cdot \frac{(W/L)_4}{(W/L)_3}$$

M_4 replaces the ideal current source under M_1

M_1 is biased by V_{BIAS} at the gate

All previous results for V_D , V_S , and $V_{BIAS,max}$ still hold — but now we must also keep M_4 in **saturation**.

Circuit Parameters

Supplies:

$$V_{DD} = 5\text{ V}, -V_{DD} = -5\text{ V}$$

Resistors:

$$R_D = 1\text{ k}\Omega$$

$$R_{REF} = 80\text{ k}\Omega$$

MOSFET Models:

$$k'_n = 1600\text{ }\mu\text{A/V}^2,$$

$$k'_p = 800\text{ }\mu\text{A/V}^2$$

$$V_{TN} = 0.5\text{ V}, \quad V_{TP} = -0.5\text{ V}$$

$$\lambda = 0.02\text{ V}^{-1}$$

Transistor Sizing:

	W/L	Role
M_1	0.5	Amplifier
M_2	1.0	PMOS bias
M_3	0.5	NMOS bias
M_4	0.5	Mirror

Operating point ($V_{BIAS} = 0$):

$$I_{REF} \approx 100\text{ }\mu\text{A}$$

$$V_{GS} \approx 1.0\text{ V}$$

$$V_S \approx -1.0\text{ V}$$

$$V_D \approx 4.9\text{ V}$$

Minimum V_{BIAS}

Keeping M_4 in Saturation

M_4 Saturation Condition

For NMOS M_4 to remain in **saturation**:

$$V_{DS4} \geq V_{GS4} - V_{TN} = V_{OV4}$$

The drain of M_4 is connected to the source of M_1 , so $V_{D4} = V_S$.

The source of M_4 is connected to $-V_{DD}$, so:

$$V_{DS4} = V_{D4} - V_{S4} = V_S - (-V_{DD}) = V_S + V_{DD}$$

Since M_4 shares V_{GS} with diode-connected M_3 (both sources at $-V_{DD}$):

$$V_{OV4} = V_{GS4} - V_{TN} = \sqrt{\frac{2I_{REF}}{k'_n(W/L)_3}}$$

The saturation condition becomes:

$$V_S + V_{DD} \geq V_{OV4}$$

Solve for Minimum V_S

From the saturation condition:

$$V_S + V_{DD} \geq V_{OV4}$$

Solving for V_S :

$$V_S \geq V_{OV4} - V_{DD}$$

Now recall our expression for V_S :

$$V_S = V_{BIAS} - V_{TN} - V_{OV1}$$

where $V_{OV1} = \sqrt{\frac{2I_{REF}}{k'_n(W/L)_1}}$ is the overdrive of M_1 .

Substituting:

$$V_{BIAS} - V_{TN} - V_{OV1} \geq V_{OV4} - V_{DD}$$

This places a **lower bound** on V_{BIAS} .

Solve for Minimum V_{BIAS}

Rearranging:

$$V_{BIAS} \geq V_{OV4} - V_{DD} + V_{TN} + V_{OV1}$$

Recognizing that $V_{TN} + V_{OV1} = V_{GS1}$:

$$V_{BIAS, \min} = V_{OV4} - V_{DD} + V_{GS1}$$

where:

$$V_{OV4} = \sqrt{\frac{2I_{REF}}{k'_n(W/L)_3}} \text{ — overdrive of the mirror transistor } M_4$$

$$V_{GS1} = V_{TN} + \sqrt{\frac{2I_{REF}}{k'_n(W/L)_1}} \text{ — gate-source voltage of } M_1$$

If V_{BIAS} drops below this value, M_4 enters **triode** and can no longer mirror I_{REF} accurately.

The Allowable Range of V_{BIAS}

Combining both constraints:

$$V_{OV4} - V_{DD} + V_{GS1} \leq V_{BIAS} \leq V_{DD} - I_{REF} \cdot R_D + V_{TN}$$

$$V_{BIAS,min} \leq V_{BIAS} \leq V_{BIAS,max}$$


Upper limit (from M_1 saturation): $V_{BIAS,max} = V_D + V_{TN}$

Lower limit (from M_4 saturation):

$$V_{BIAS,min} = V_{OV4} - V_{DD} + V_{GS1}$$

Both M_1 and the mirror transistor M_4 must remain in saturation for the circuit to function correctly.

SPICE Simulation: V_S vs V_{BIAS}

 


V_S tracks V_{BIAS} linearly in saturation. Red X marks $V_{BIAS} = V_D - V_{TN}$ — beyond this, M_1 enters triode.

The Differential Pair

Two MOSFETs Sharing One Current Source

The Differential Pair Circuit

 

The Differential Pair

Both gates tied to V_{BIAS} — this is the **bias point** of a differential pair

Each transistor has its own drain resistor (R_{D1} , R_{D2})

Sources tied together at V_S ; current source sinks $I_{REF} = I_{D1} + I_{D2}$

With matched transistors and $V_{G1} = V_{G2}$, the current splits equally:


$$I_{D1} = I_{D2} = \frac{I_{REF}}{2}$$

The drain voltages are:

$$V_{D1} = V_{DD} - \frac{I_{REF}}{2} \cdot R_{D1}, \quad V_{D2} = V_{DD} - \frac{I_{REF}}{2} \cdot R_{D2}$$

This is the foundation of the **differential amplifier**. Next step: apply different voltages to each gate and see how the current steers.

SPICE Simulation: V_{OUT} vs V_{BIAS}

 


With both gates tied to V_{BIAS} , $V_{OUT} = V_{D1} - V_{D2} = 0$ for all V_{BIAS} .
Matched transistors split I_{REF} equally — no differential output.

BJT Differential Pair

Same Analysis, Different Device

The BJT Differential Pair Circuit

 

The BJT Differential Pair

Both bases tied to V_{BIAS} — identical to the MOSFET case

Each transistor has its own collector resistor (R_{C1} , R_{C2})

Emitters tied together at V_E ; current source sinks $I_{REF} = I_{C1} + I_{C2}$

With matched transistors and $V_{B1} = V_{B2}$, the current splits equally:


$$I_{C1} = I_{C2} = \frac{I_{REF}}{2}$$

The collector voltages are:

$$V_{C1} = V_{CC} - \frac{I_{REF}}{2} \cdot R_{C1}, \quad V_{C2} = V_{CC} - \frac{I_{REF}}{2} \cdot R_{C2}$$

Key difference: BJT has $V_E = V_{BIAS} - V_{BE}$ (fixed ≈ 0.7 V drop)
vs. MOSFET $V_S = V_{BIAS} - V_{GS}$ (depends on $\sqrt{I_D}$).

 SPICE Simulation: BJT V_{OUT} vs V_{BIAS}



With both bases tied to V_{BIAS} , $V_{OUT} = V_{C1} - V_{C2} = 0$ for all V_{BIAS} . Matched transistors split I_{REF} equally — same result as the MOSFET pair.

Lecture 18 Summary

Single NMOS with current source biasing: $V_S = V_{BIAS} - V_{GS}$,

$$V_D = V_{DD} - I_{REF} \cdot R_D$$

Maximum V_{BIAS} (keeping M_1 in saturation): $V_{BIAS,max} = V_{DD} - I_{REF} \cdot R_D + V_{TN}$

MOSFET current mirror replaces the ideal current source:

PMOS + R_{REF} + NMOS bias network sets I_{REF} ; mirror transistor copies the current

Minimum V_{BIAS} (keeping mirror in saturation): $V_{BIAS,min} = V_{OV4} - V_{DD} + V_{GS1}$

MOSFET differential pair: two matched MOSFETs sharing a tail current source

With equal gate voltages: $I_{D1} = I_{D2} = I_{REF}/2$ and $V_{OUT} = 0$

BJT differential pair: same topology with NPN transistors

With equal base voltages: $I_{C1} = I_{C2} = I_{REF}/2$ and $V_{OUT} = 0$

Key difference: $V_E = V_{BIAS} - V_{BE}$ (fixed) vs. $V_S = V_{BIAS} - V_{GS}$
($\sqrt{I_D}$ -dependent)

Next: Apply different voltages to each gate/base and analyze current steering and differential gain.