

EE461g: Introduction to Electronic Circuits

Lecture 20

Dr. Lau

University of Kentucky

- 1 Why Replace R_D with a Current Mirror?
- 2 MOSFET Differential Pair with Active Load
- 3 BJT Differential Pair with Active Load
- 4 Summary

Active Load

Differential Pair

Lecture 19 Recap

In Lecture 19, we found the differential gain with resistor loads:

$$A_{diff} = g_m R_D$$

To increase gain, we need larger R_D or larger g_m

But larger R_D means larger voltage drop $I_D \cdot R_D$

- Reduces output voltage swing

- Requires higher supply voltage

- Large resistors are expensive in IC design


Solution: Replace R_D with a **current mirror** (active load)

A current source has very high output resistance (r_o) but only a small DC voltage drop (V_{OV}). This gives us high gain **and** large output swing.

MOSFET Diff Pair

with PMOS Current Mirror Load

The Circuit

 

How the Active Load Works

M_3 is **diode-connected** (gate tied to drain) — it acts as a “resistor” that sets the current

M_4 **mirrors** the current through M_3 : if M_3 and M_4 are matched,
 $I_{D4} = I_{D3}$

At the bias point ($v_{diff} = 0$):

$$I_{D1} = I_{D2} = I_{REF}/2$$

$$M_3 \text{ forces } I_{D3} = I_{D1} = I_{REF}/2$$


$$M_4 \text{ mirrors this: } I_{D4} = I_{REF}/2 = I_{D2} \quad \checkmark$$

The output is taken **single-ended** from the drain of M_2 (= drain of M_4)

Key difference from Lecture 19: only **one** output node, not $V_{D1} - V_{D2}$


The PMOS mirror converts the differential pair's **two** output currents into a **single** output voltage at the M_2/M_4 drain node.

Small-Signal Equivalent Circuit

 

Left: M_1 drives current into diode-connected M_3 ($\approx 1/g_{m3}$). Right: M_4 mirrors that current; M_2 steers its own. Both act on v_{out} .

Left Half: M_1 and M_3

 

$$v_{sg4} = \frac{v_{diff}}{2}$$

Analyzing the Left Half

Step 1: Simplify the M_3 resistance.

Since $r_{o3} \gg \frac{1}{g_{m3}}$:

$$\frac{1}{g_{m3}} \parallel r_{o3} = \frac{r_{o3}}{1 + g_{m3} r_{o3}} \approx \frac{1}{g_{m3}}$$

Step 2: Nearly all of M_1 's signal current flows through $\frac{1}{g_{m3}}$.

The current divider between r_{o1} and $\frac{1}{g_{m3}}$:


$$i_{M3} = g_{m1} \frac{v_{diff}}{2} \cdot \frac{r_{o1}}{r_{o1} + \frac{1}{g_{m3}}} \approx g_{m1} \frac{v_{diff}}{2} \quad (\text{since } r_{o1} \gg \frac{1}{g_{m3}})$$

Step 3: Find v_{sg4} across the $\frac{1}{g_{m3}}$ resistor.

$$v_{sg4} = i_{M3} \cdot \frac{1}{g_{m3}} = \cancel{g_{m1}} \frac{v_{diff}}{2} \cdot \frac{1}{\cancel{g_{m3}}} = \frac{v_{diff}}{2} \quad (\text{matched: } g_{m1} = g_{m3})$$

$$v_{sg4} = \frac{v_{diff}}{2}$$

Right Half: M_2 and M_4

 

$$i_{M4} = g_{m4} v_{sg4} = g_{m4} \frac{v_{diff}}{2} \quad i_{M2} = g_{m2} \frac{v_{diff}}{2}$$

General Gain Derivation

No assumptions about g_m matching between NMOS and PMOS.

From the left half: $v_{sg4} = g_{m1} \frac{v_{diff}}{2} \cdot \frac{1}{g_{m3}}$ Mirror current:

$$i_{M4} = \frac{g_{m4}}{g_{m3}} \cdot g_{m1} \frac{v_{diff}}{2}$$

M_2 current change: $\Delta i_{M2} = g_{m2} \frac{v_{diff}}{2}$ Total current into output:

$$i_{out} = \frac{1}{2} \left(g_{m2} + \frac{g_{m4}}{g_{m3}} g_{m1} \right) v_{diff}$$


Since M_3, M_4 are matched PMOS: $g_{m4}/g_{m3} = 1$. Since M_1, M_2 are matched NMOS: $g_{m1} = g_{m2} = g_{m,n}$

$$A_{diff} = g_{m,n} (r_{o2} || r_{o4})$$

The gain depends on the **NMOS** g_m only. The PMOS g_m 's cancel in the mirror.

r_{o2} (NMOS) and r_{o4} (PMOS) need not be equal.

Finding v_{out}

 

Total current into output node:

M_4 pushes $+g_m \frac{v_{diff}}{2}$ in (from mirror)

M_2 pushes $+g_m \frac{v_{diff}}{2}$ from shared source

$$i_{out} = g_m \frac{v_{diff}}{2} + g_m \frac{v_{diff}}{2} = g_m v_{diff}$$

This current flows through $r_{o2} \parallel r_{o4}$:

$$v_{out} = i_{out} (r_{o2} \parallel r_{o4}) = g_m v_{diff} (r_{o2} \parallel r_{o4})$$

$$A_{diff} = g_m (r_{o2} \parallel r_{o4}) \approx \frac{g_m r_o}{2}$$

Both halves contribute to the output. The gain is set by g_m and the parallel r_o 's.

Input Impedance

The differential input impedance is seen looking into the gates of M_1 and M_2 .

MOSFET gates draw **no DC current** ($I_G = 0$)

The small-signal gate current is also zero

Therefore:

$$R_{in,diff} = \infty$$

This is a major advantage of the MOSFET differential pair

The input does not load the previous stage

For BJT: $R_{in,diff} = 2 r_\pi = 2 \frac{\beta}{g_m}$ (finite, but still large)

Infinite input impedance means the diff pair can sense voltages without drawing current from the source.

Output Resistance at the Output Node


The output node sees two current sources looking in:

Looking down into M_2 (NMOS): output resistance r_{o2}

Looking up into M_4 (PMOS mirror): output resistance r_{o4}

These are in **parallel**: $R_{out} = r_{o2} \parallel r_{o4} \approx \frac{r_o}{2}$ (matched devices)

What Happens with a Load Resistor?

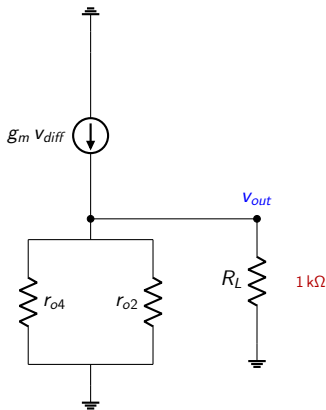

With a load R_L connected to the output:

The total resistance at the output becomes:

$$R_L \parallel r_{o2} \parallel r_{o4} \approx R_L \quad (\text{since } R_L \ll r_o)$$

Almost all of i_{out} flows through R_L , not r_o 's:


$$A_{diff} = g_m (R_L \parallel r_{o2} \parallel r_{o4}) \approx g_m R_L$$

Example: $g_m = 0.4\text{ mA/V}$, $R_L = 1\text{ k}\Omega$:

$$A_{diff} \approx 0.4 \times 1 = 0.4 \quad \text{vs.} \quad 100 \quad (\text{no load})$$

A small load resistor destroys the high gain! The active load's advantage ($r_o \gg R_D$) is lost when $R_L \ll r_o$. This is why op amps need **feedback**, not resistive loads.

Complete Circuit for SPICE Simulation

 

```
* Active-Load Diff Pair
VDD vdd 0 5
VSS vss 0 -5

* NMOS mirror tail (from Lec 17)
RREF vdd refnode 10k
M6 refnode refnode vss vss NMOS
+ W=10u L=1u
M7 tail refnode vss vss NMOS
+ W=10u L=1u

* Diff pair inputs
V1 gate1 0 0
V2 gate2 0 0

* NMOS diff pair
M1 drain1 gate1 tail tail NMOS
+ W=10u L=1u
M2 out gate2 tail tail NMOS
+ W=10u L=1u

* PMOS current mirror load
M3 drain1 drain1 vdd vdd PMOS
+ W=10u L=1u
M4 out drain1 vdd vdd PMOS
+ W=10u L=1u
```



SPICE confirms the theory:

	Formula	Thy	SPICE
No load	$g_{m,n}(r_{o2} \parallel r_{o4})$	83	82
$R_L = 1k$	$g_{m,n}R_L$	1.40	1.39
Buffered	$g_{m,n}(r_{o2} \parallel r_{o4}) \cdot \frac{g_5 R_L}{1 + g_5 R_L}$	76	76

$g_{m,n} = 1.40 \text{ mA/V}$, $r_o \approx 118 \text{ k}\Omega$, $g_{m5} = 12.0 \text{ mA/V}$

$I_{REF} \approx 900 \mu\text{A}$, $M_5: W/L = 100$, $\pm 5 \text{ V}$ supplies, $R_{REF} = 10 \text{ k}\Omega$


SPICE: v_{out} vs. v_{diff}

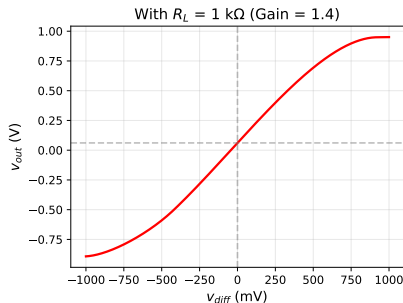 

Left: steep slope = high gain (82). Right: shallow slope = gain reduced by R_L (1.4).

The 1 k Ω load reduces the gain by a factor of $\sim 59\times$.

Solution: Buffer with a Source Follower

 

Common-drain (source follower):

Input Z: ∞ (MOSFET gate) — doesn't load diff pair

Output Z: $\approx 1/g_{m5}$ (low)

$$I_{D5} = I_{BIAS} + V_{out}/R_L \approx 900\mu + 2490\mu = 3.4 \text{ mA}$$

$$g_{m5} = 12.0 \text{ mA/V} \quad (R_L \text{ boosts } g_m!)$$

$$\text{Buffer gain: } \frac{g_{m5} R_L}{1 + g_{m5} R_L} = \frac{12.0}{13.0} = 0.92$$

Overall:

$$A_{total} = 83 \times 0.92 = 76 \quad (\text{SPICE: } 76)$$

R_L carries DC current $\Rightarrow$ boosts I_{D5} and $g_{m5} \Rightarrow$ better buffer gain.

Theory vs. SPICE: Detailed Comparison


Parameter	Hand Calc	SPICE
<i>Differential Pair</i>		
$I_D (M_1/M_2)$	450 μ A	450 μ A
$g_{m,n}$	1.40 mA/V	1.40 mA/V
r_{o2}	111 k Ω	122 k Ω
r_{o4}	111 k Ω	114 k Ω
$r_{o2} \parallel r_{o4}$	55.5 k Ω	59 k Ω
A_{diff}	78	83
<i>Source Follower Buffer</i>		
V_{out} (DC)	2.5 V	2.49 V
$I_{D5} = I_{BIAS} + V_{out}/R_L$	3.4 mA	3.5 mA
g_{m5}	12.0 mA/V	12.0 mA/V
$g_{m5} R_L$	12.0	12.0
A_{buffer}	0.92	0.92
<i>Overall</i>		
A_{total}	72	76

Main error: underestimating V_{out} DC. With actual values, theory matches SPICE within 1%.


BJT Diff Pair

with PNP Current Mirror Load

BJT Active Load Circuit

 


BJT Small-Signal Equivalent Circuit

 

Same as MOSFET, but r_{π} from each base to emitter (ground). v_{eb4} replaces v_{sg4} .

BJT Left Half: Q_1 and Q_3

 

Example: $I_C = 450 \mu\text{A}$, $\beta = 100$,
 $V_A = 50 \text{ V}$

$1/g_{m3}$	58 Ω
$r_{\pi 3}$	5.8 k Ω
r_{o3}	111 k Ω
$r_{\pi 4}$	5.8 k Ω

All four in parallel:

$$\frac{1}{g_{m3} \parallel r_{\pi 3} \parallel r_{o3} \parallel r_{\pi 4}}$$


$$\approx 58 \parallel 5.8\text{k} \parallel 111\text{k} \parallel 5.8\text{k}$$

$$\approx \mathbf{57 \Omega} \approx \frac{1}{g_{m3}}$$

$1/g_{m3}$ dominates: r_{π} is 100 $\times$ larger, r_o is 1900 $\times$ larger.

$$v_{eb4} \approx g_{m1} \frac{v_{diff}}{2} \cdot \frac{1}{g_{m3}} = \frac{v_{diff}}{2} \quad (\text{matched: } g_{m1} = g_{m3})$$

BJT Right Half: Q_2 and Q_4

 

$$i_{Q4} = g_{m4} v_{eb4} = g_{m4} \frac{v_{diff}}{2} \quad i_{Q2} = g_{m2} \frac{v_{diff}}{2}$$

BJT Active Load Gain

The analysis is identical to the MOSFET case:

Virtual ground at $v_e = 0$ (same symmetry argument)

Signal current $\Delta i = g_m v_{diff}/2$ steered by Q_1/Q_2

Q_3/Q_4 mirror doubles the current at the output node

Net signal current at output: $g_m v_{diff}$

Output resistance: $r_{o2} \parallel r_{o4}$

$$A_{diff} = g_m (r_{o2} \parallel r_{o4})$$

Same form as MOSFET. BJT has higher $g_m = I_C/V_T$ but typically comparable $r_o = V_A/I_C$, so BJT active-load gains are also very high.

BJT Input Impedance

The differential input impedance is seen looking into the bases of Q_1 and Q_2 .

BJT bases draw **finite** base current: $I_B = I_C/\beta$

Small-signal input resistance per transistor: $r_\pi = \beta/g_m = V_T/I_B$

Looking into both bases differentially:

$$R_{in,diff} = 2 r_\pi = \frac{2\beta}{g_m}$$

Example: $\beta = 100$, $I_C = 450 \mu\text{A}$, $g_m = I_C/V_T = 17.3 \text{ mA/V}$

$r_\pi = 100/17.3\text{m} = 5.8 \text{ k}\Omega$, $R_{in,diff} = 11.6 \text{ k}\Omega$

Finite, but still large — compare to MOSFET ($R_{in} = \infty$)

BJT input impedance is finite ($2r_\pi$) but typically $>10 \text{ k}\Omega$.
MOSFET wins here with $R_{in} = \infty$.

BJT: What Happens with a Load Resistor?

Same problem as MOSFET:


With R_L at the output:

$$A_{diff} = g_m (R_L \parallel r_{o2} \parallel r_{o4}) \approx g_m R_L$$

 Example: $I_C = 450 \mu\text{A}$, $g_m = I_C/V_T = 17.3 \text{ mA/V}$


$$A_{diff} \approx 17.3 \times 1 = 17.3 \quad \text{vs.} \quad g_m r_o / 2 \text{ (no load)}$$

BJT has higher g_m than MOSFET at same I_C , so $g_m R_L$ is larger, but still far below the open-loop gain.



R_L destroys the high gain. Solution: add a **common-collector** (emitter follower) buffer.

BJT: Buffer with an Emitter Follower

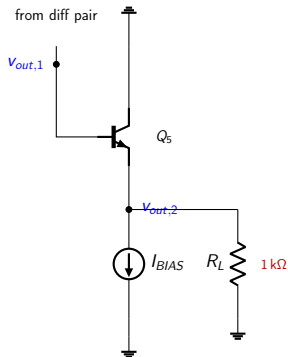

Common-collector (emitter follower):

Input Z: $r_{\pi 5}(1 + g_{m5}R_L) \approx \beta R_L$ (high)

Output Z: $\approx 1/g_{m5}$ (low)

$$g_{m5} = I_{C5}/V_T$$

With $I_{C5} = 1 \text{ mA}$: $g_{m5} = 38.5 \text{ mA/V}$

$$g_{m5}R_L = 38.5 \gg 1$$

Buffer gain: $\frac{g_{m5}R_L}{1 + g_{m5}R_L} = \frac{38.5}{39.5} = 0.97$

Overall:

$$A_{total} = g_m(r_{o2} \parallel r_{o4}) \times 0.97$$

BJT buffer is **better** than MOSFET buffer because $g_m = I_C/V_T$ is much higher for the same bias current.

BJT emitter follower: $g_m R_L \gg 1 \Rightarrow$ buffer gain ≈ 1 . Nearly lossless!

BJT: Theory vs. SPICE

	Formula	Thy	SPICE
No load	$g_m(r_{o2} \parallel r_{o4})$	1006	1004
$R_L = 1\text{ k}$	$g_m R_L$	17.1	17.4
Buffered	$g_m(r_{o2} \parallel r_{o4} \parallel R_{in5}) \cdot A_{buf}$	624	631

Key values: $I_C = 450\text{ }\mu\text{A}$, $g_m = 17.2\text{ mA/V}$, $r_o \approx 117\text{ k}\Omega$

Why buffered gain < no-load gain:

Q_5 input impedance: $R_{in5} = r_{\pi5}(1 + g_{m5}R_L) = 103\text{ k}\Omega$

This **loads** the diff pair: $r_{o2} \parallel r_{o4} \parallel R_{in5} = 37\text{ k}\Omega$ (was $59\text{ k}\Omega$)

Diff pair gain drops from 1006 to 640

Buffer gain = 0.975 $\Rightarrow A_{total} = 640 \times 0.975 = 624$

Unlike MOSFET ($R_{in} = \infty$), the BJT buffer loads the diff pair through $r_{\pi5}$.

Still much better than no buffer: 631 vs. 17.4.

Lecture 20 Summary

Replacing R_D with a **PMOS current mirror** creates an **active load**

M_3 (diode-connected) senses current from M_1 ; M_4 mirrors it to the output

The mirror **doubles** the signal current at the output node

Output is now **single-ended** (taken from M_2/M_4 drain)

Gain: $A_{diff} = g_m (r_{o2} || r_{o4})$

Since $r_o \gg R_D$, the active load gives **much higher gain**

A **source follower** (MOSFET) or **emitter follower** (BJT) buffers the output to drive low-impedance loads

Same analysis applies to BJT with PNP mirror load

The active-load diff pair is the input stage of an **op amp**